

EE 446
Computer Architecture II

Lecture
(Week 1)

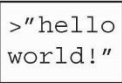

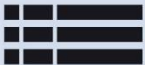
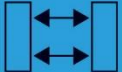
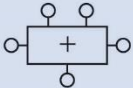

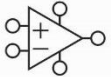
 
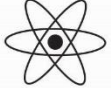
Arm Microarchitecture
(single cycle)

METU EE446 Lecture notes v1.3

Based on:
Digital Design and Computer Architecture: ARM® Edition, Harris&Harris


Topics

- **Introduction**
- **Performance Analysis**
- **Single-Cycle Processor**
- Multicycle Processor
- Pipelined Processor
- Advanced Microarchitecture

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction

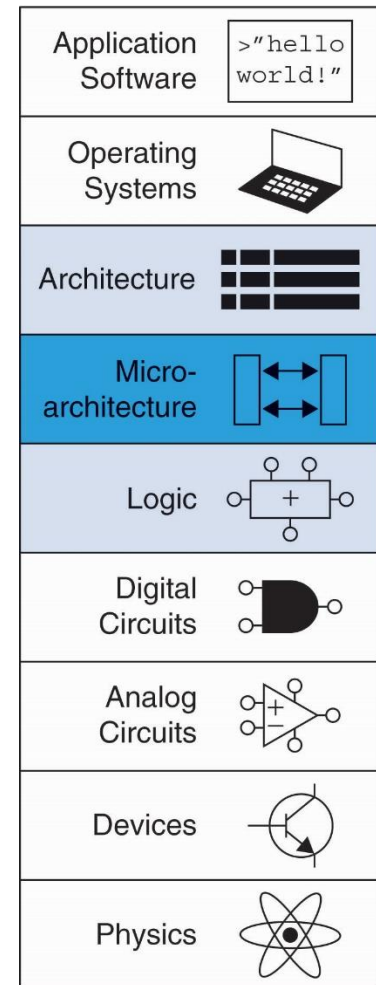- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals



Microarchitecture

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken up into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

Processor Performance

- **Program execution time**

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance

ARM Processor


- Consider **subset** of ARM instructions:
 - **Data-processing instructions:**
 - **ADD, SUB, AND, ORR**
 - with register and immediate Src2, but **no shifts**
 - **Memory instructions:**
 - **LDR, STR**
 - with **positive immediate offset**
 - **Branch instructions:**
 - **B**

Architectural State Elements

Determines everything about a processor:

- Architectural state:
 - 16 registers (including PC)
 - Status register
- Memory

ARM Architectural State Elements

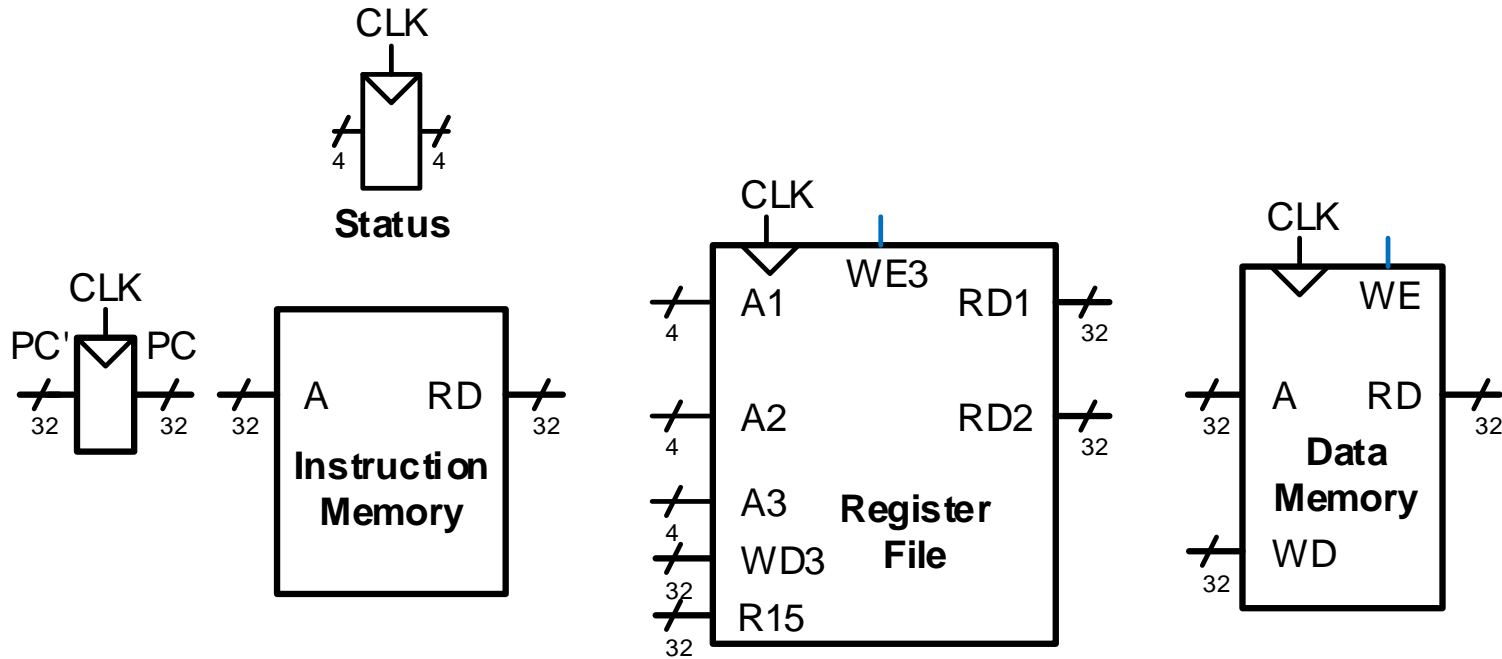

The instruction memory, register file, and data memory are all read combinationally.

Microarchitecture Design Styles

- single-cycle microarchitecture
- multi-cycle microarchitecture
- pipelined microarchitecture

Single-Cycle ARM Processor

Single-cycle microarchitecture:

- It executes an entire instruction in one cycle.
- It is easy to explain and has a simple control unit.
- Because it completes the operation in one cycle, it does not require any non-architectural state.
- However, the cycle time is limited by the slowest instruction.
- Moreover, the processor requires separate instruction and data memories, which is generally unrealistic.

Single-Cycle ARM Processor

- Datapath
- Control


Single-Cycle ARM Processor

- **Datapath**
- Control

Single-Cycle ARM Processor


- **Datapath:** start with LDR instruction

 - **Example:** LDR R1, [R2, #5]
LDR Rd, [Rn, imm12]





Single-Cycle Datapath: LDR fetch


STEP 1: Fetch instruction

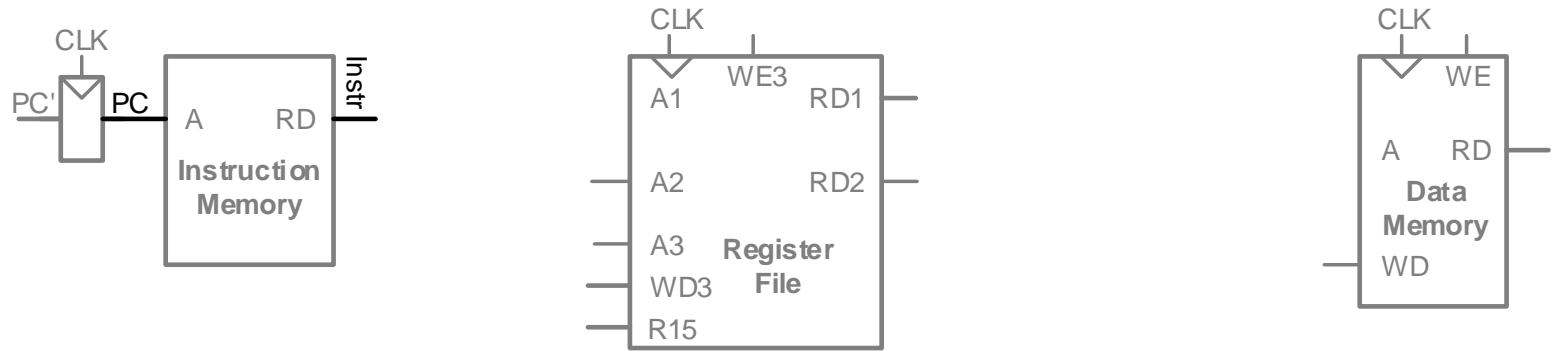

Single-Cycle Datapath: LDR Reg Read



STEP 2: Read source operands from RF

 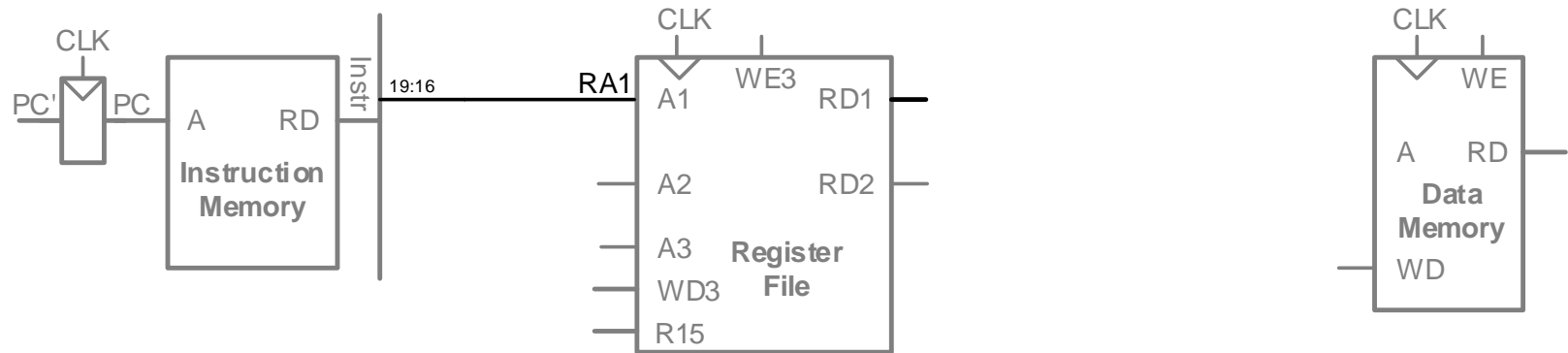

 



Single-Cycle Datapath: LDR Address

STEP 4: Compute the memory address

 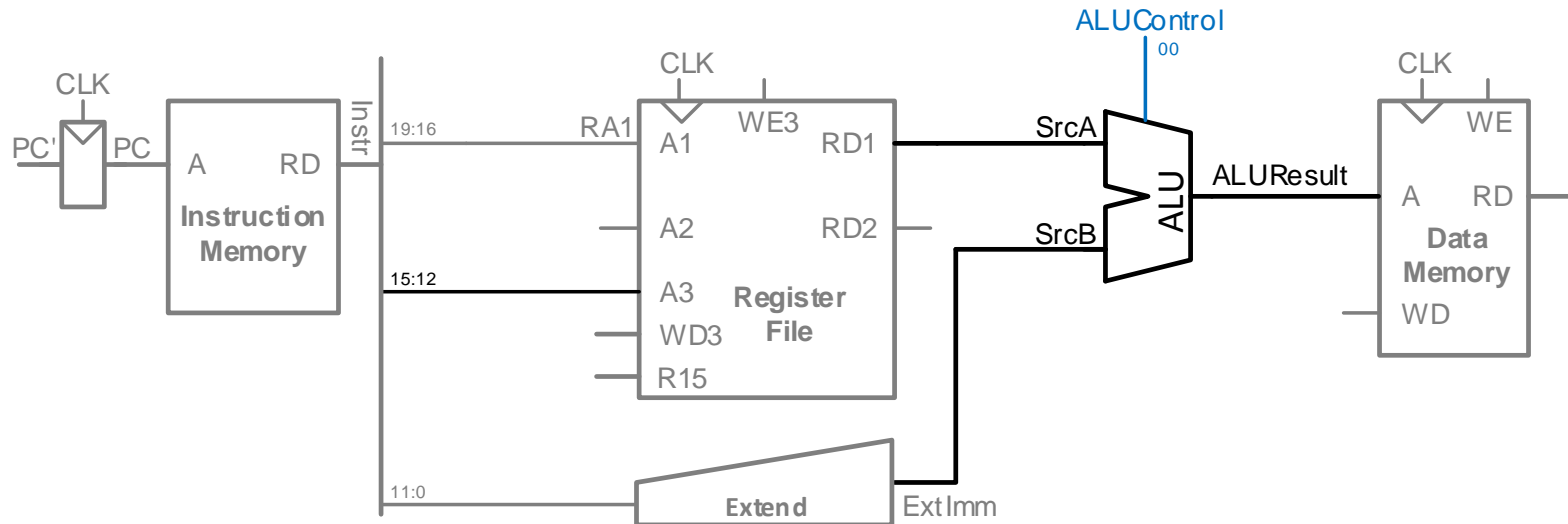


Single-Cycle Datapath: LDR Mem Read

 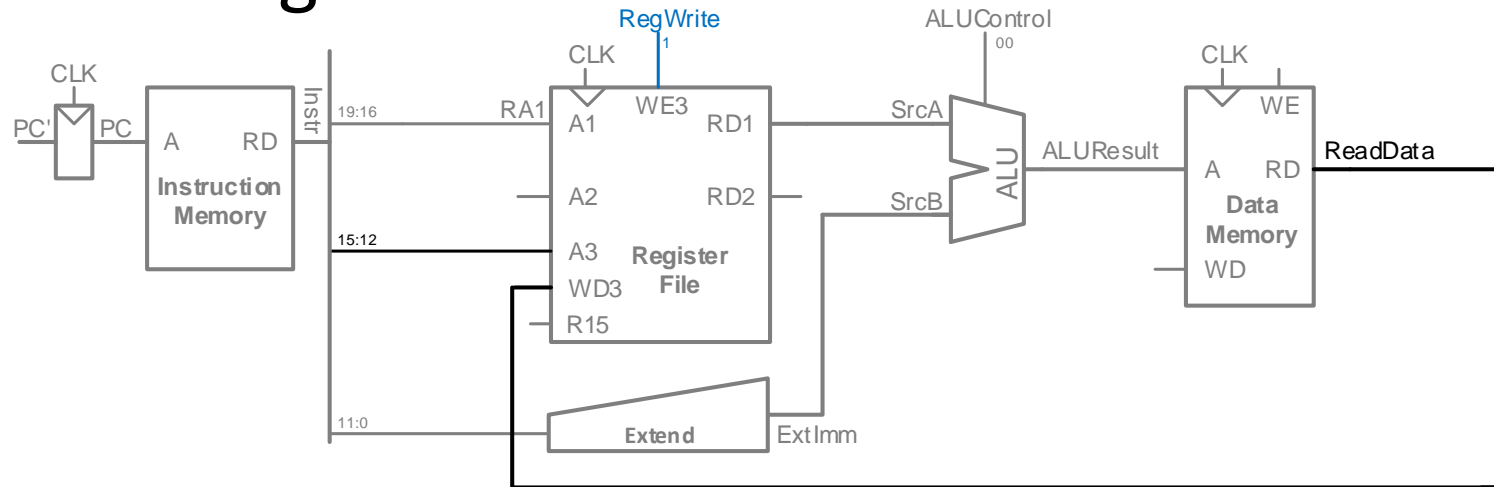STEP 5: Read data from memory and write it back to register file



Single-Cycle Datapath: PC Increment

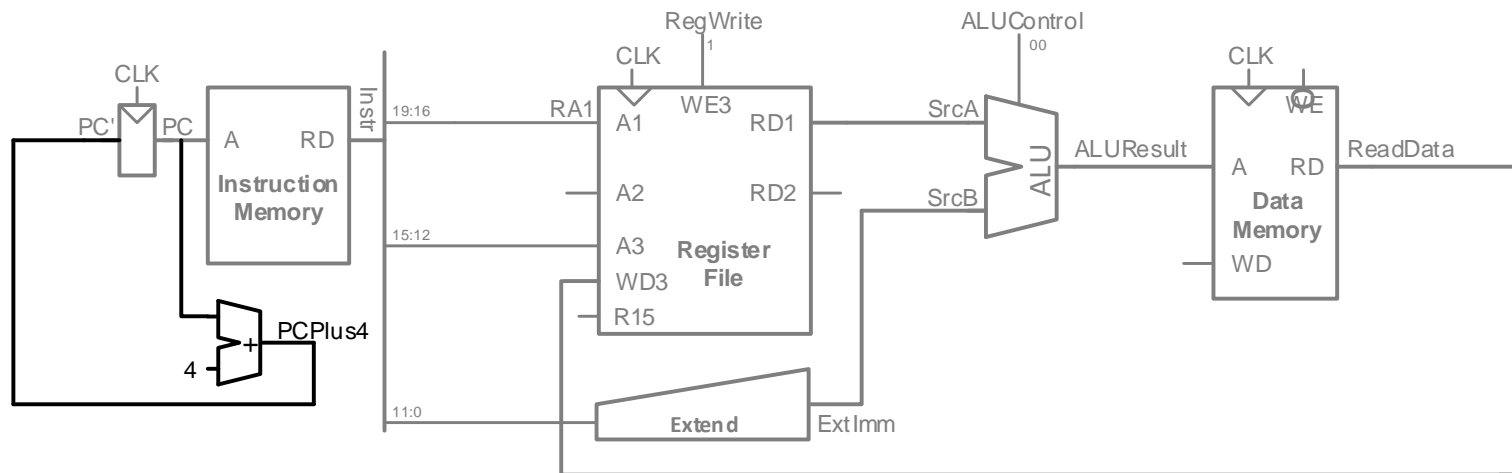
STEP 6: Determine address of next instruction
(Increment the PC by one word)



Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction

Read or write program counter as R15

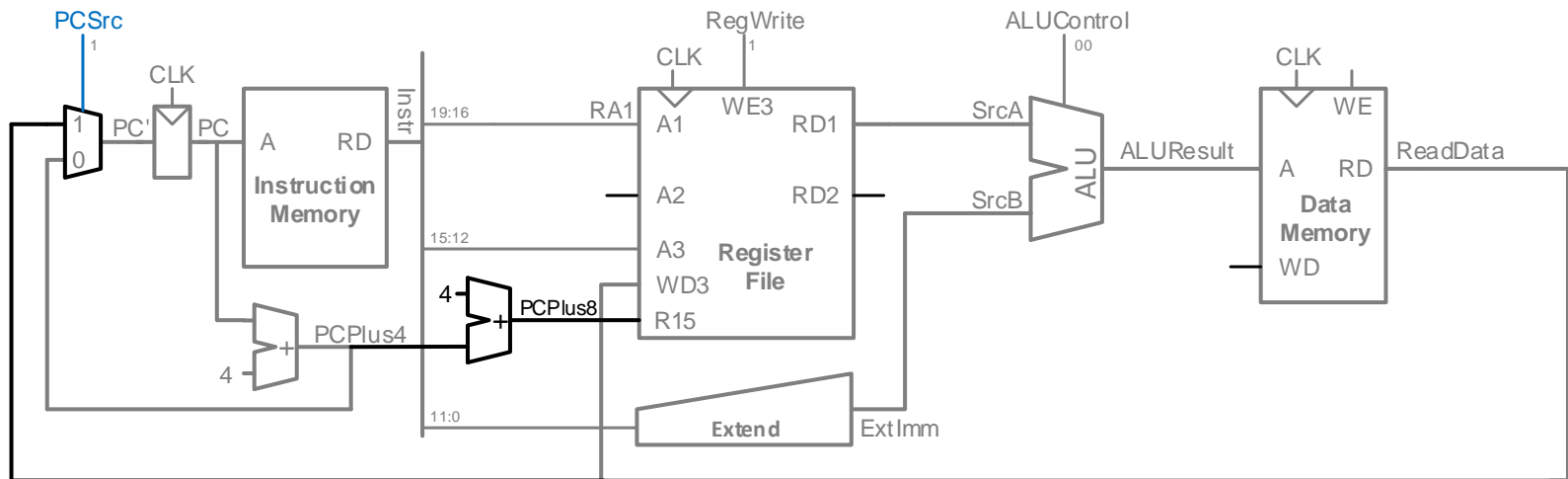


- Note: reading register R15 returns $PC + 8$.

Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction

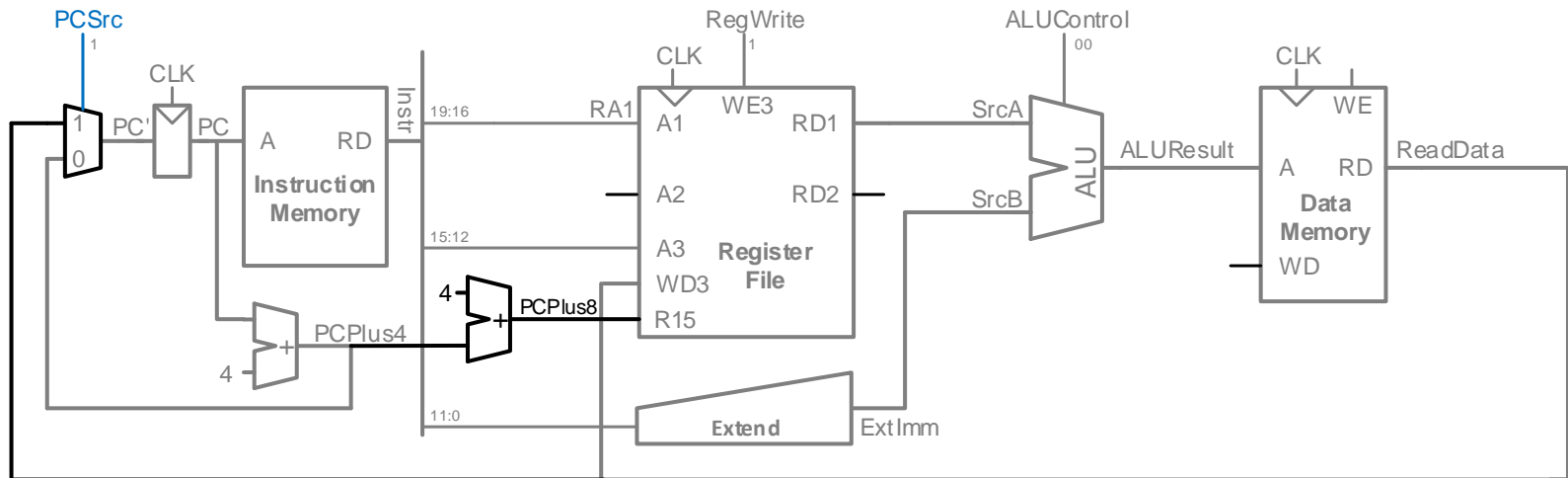
- **Source:** R15 must be available in Register File
 - **PC** is read as the current **PC plus 8**



Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction


 
- **Source:** R15 must be available in Register File
 - **PC** is read as the current **PC plus 8**
- **Destination:** Be able to write result to PC



Single-Cycle Datapath: STR

Expand datapath to handle STR:


- Write data in Rd to memory

 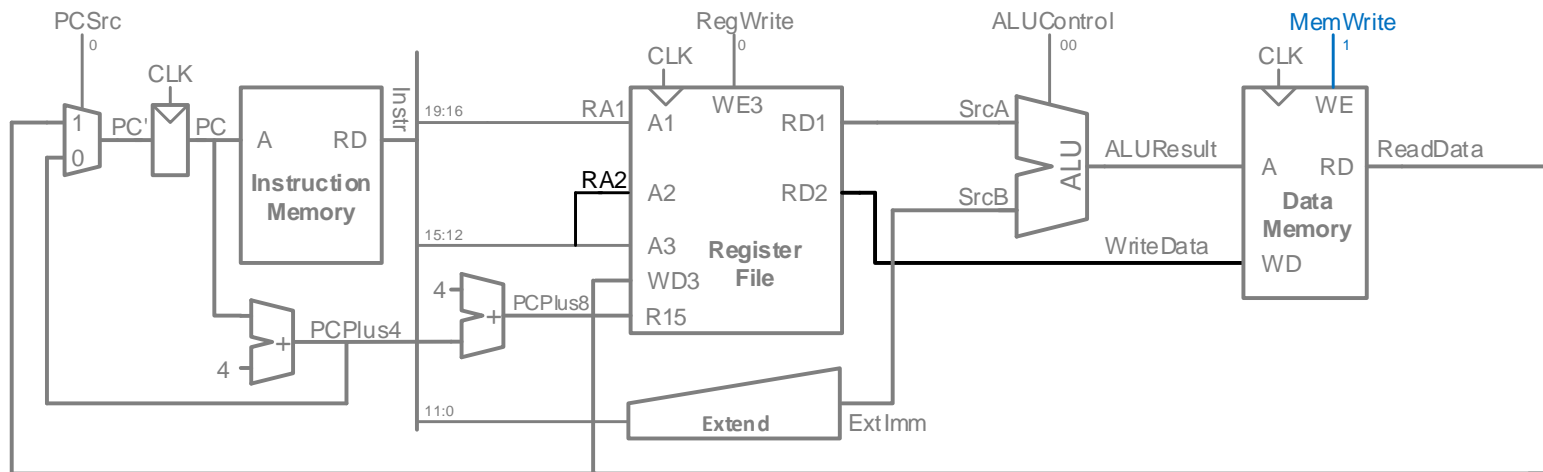

Single-Cycle Datapath: Data-processing

With **immediate** Src2:

 - Read from R_n and $Imm8$ ($ImmSrc$ chooses the zero-extended $Imm8$ instead of $Imm12$)
- Write $ALUResult$ to register file
- Write to R_d




ADD R_d , R_n , imm8

Single-Cycle Datapath: Data-processing

With **immediate Src2**:

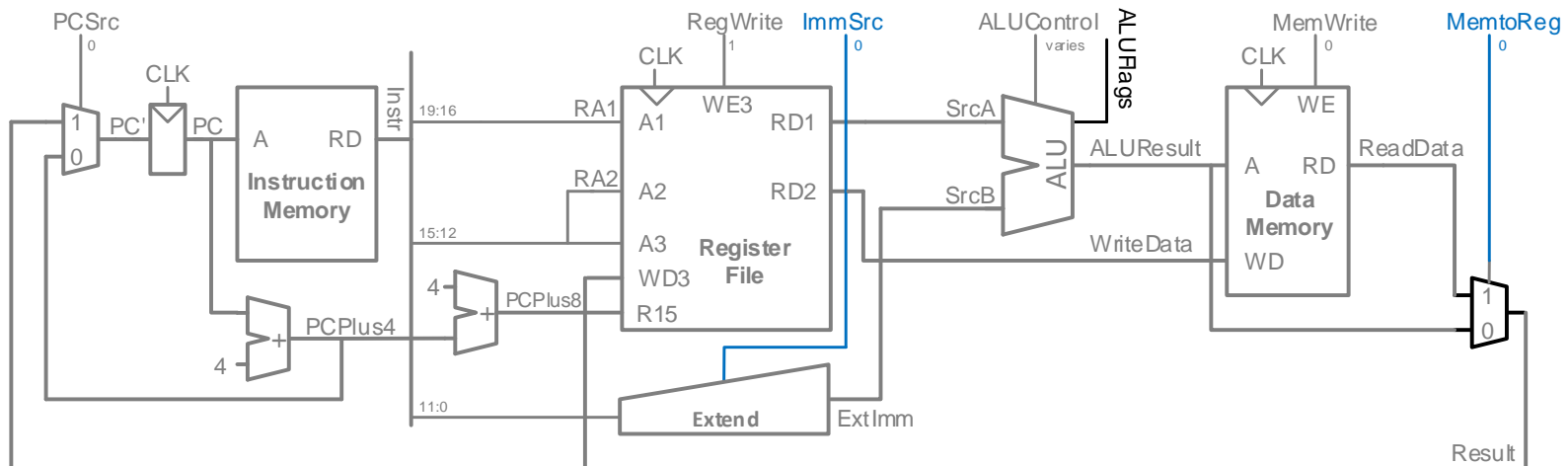- Read from R_n and $Imm8$ (*ImmSrc* chooses the zero-extended $Imm8$ instead of $Imm12$)
- Write *ALUResult* to register file
- Write to R_d




ADD R_d , R_n , $imm8$

Single-Cycle Datapath: Data-processing

With **register Src2**:

 - Read from R_n and R_m (instead of $Imm8$)
- Write *ALUResult* to register file
- Write to R_d




ADD R_d , R_n , R_m

Single-Cycle Datapath: Data-processing

With **register Src2**:

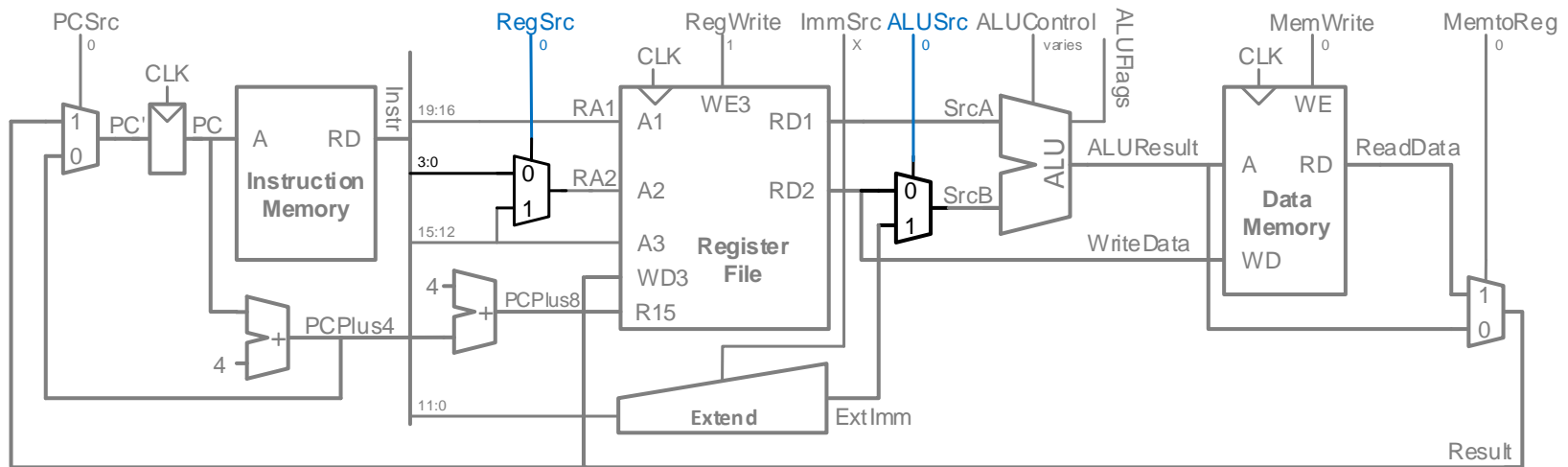- Read from R_n and R_m (instead of $Imm8$)
- Write $ALUResult$ to register file
- Write to R_d




ADD R_d, R_n, R_m

Single-Cycle Datapath: B


Calculate branch target address:

$$\text{BTA} = (\text{ExtImm}) + (\text{PC} + 8)$$

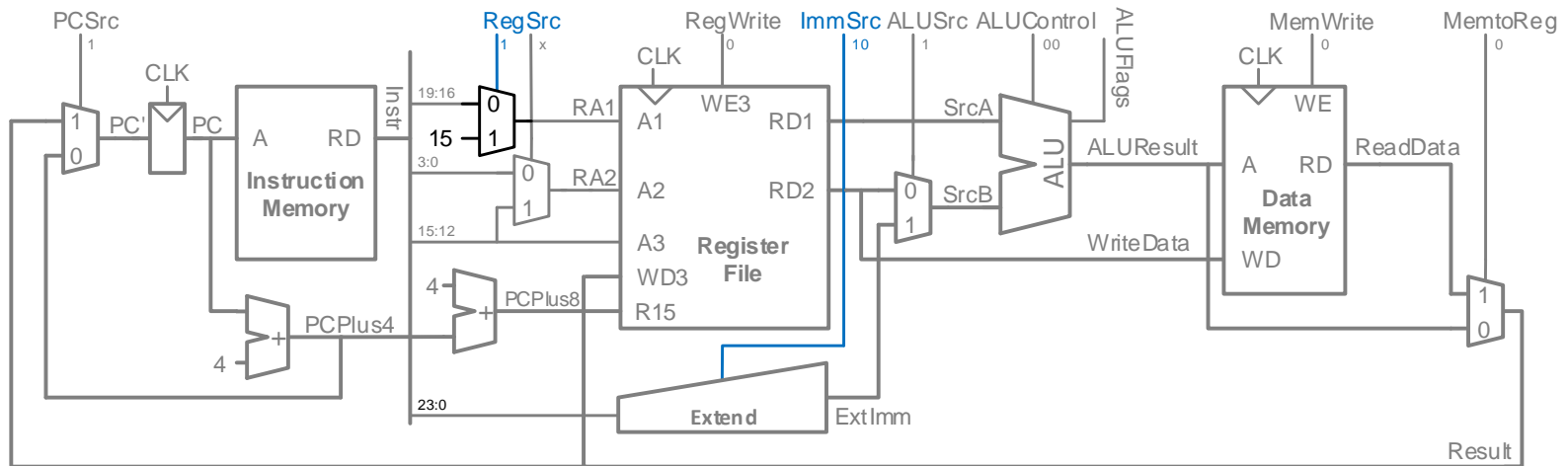$\text{ExtImm} = \text{Imm24} \ll 2$ and sign-extended




Branch

 

funct


B Label

Single-Cycle Datapath: ExtImm

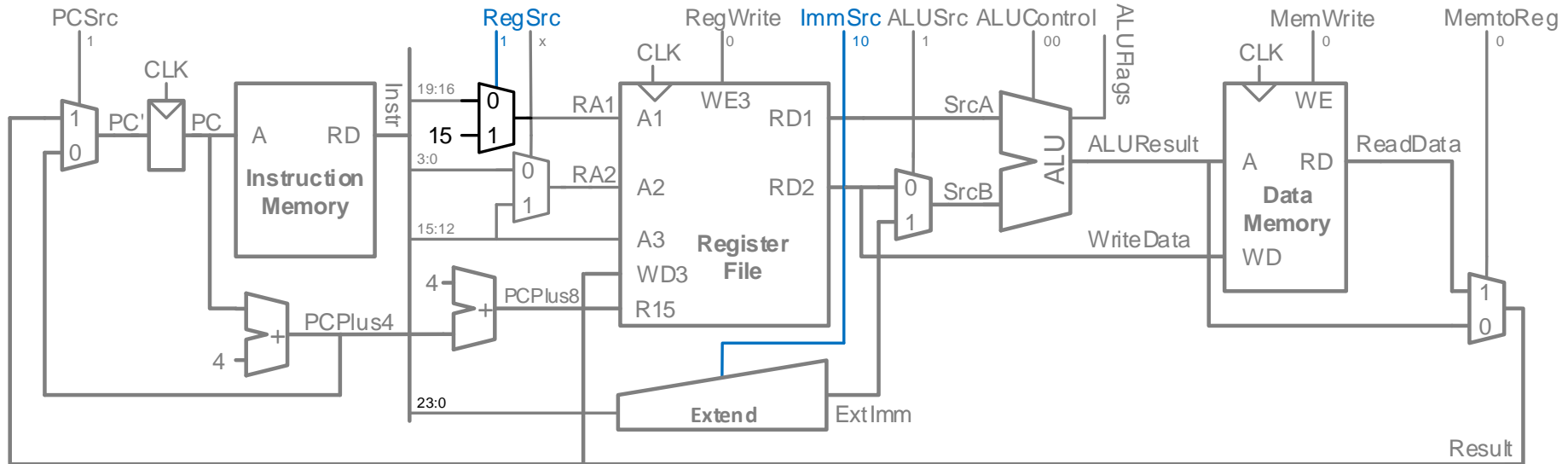


ImmSrc _{1:0}	ExtImm	Description
00	{24'b0, Instr _{7:0} }	Zero-extended <i>imm8</i> (for data-processing)
01	{20'b0, Instr _{11:0} }	Zero-extended <i>imm12</i> (for LDR/STR)
10	{6{Instr ₂₃ }, Instr _{23:0} , 2'b0}	Sign-extended <i>imm24</i> (multiplied by 4 for B)


Single-Cycle ARM Processor

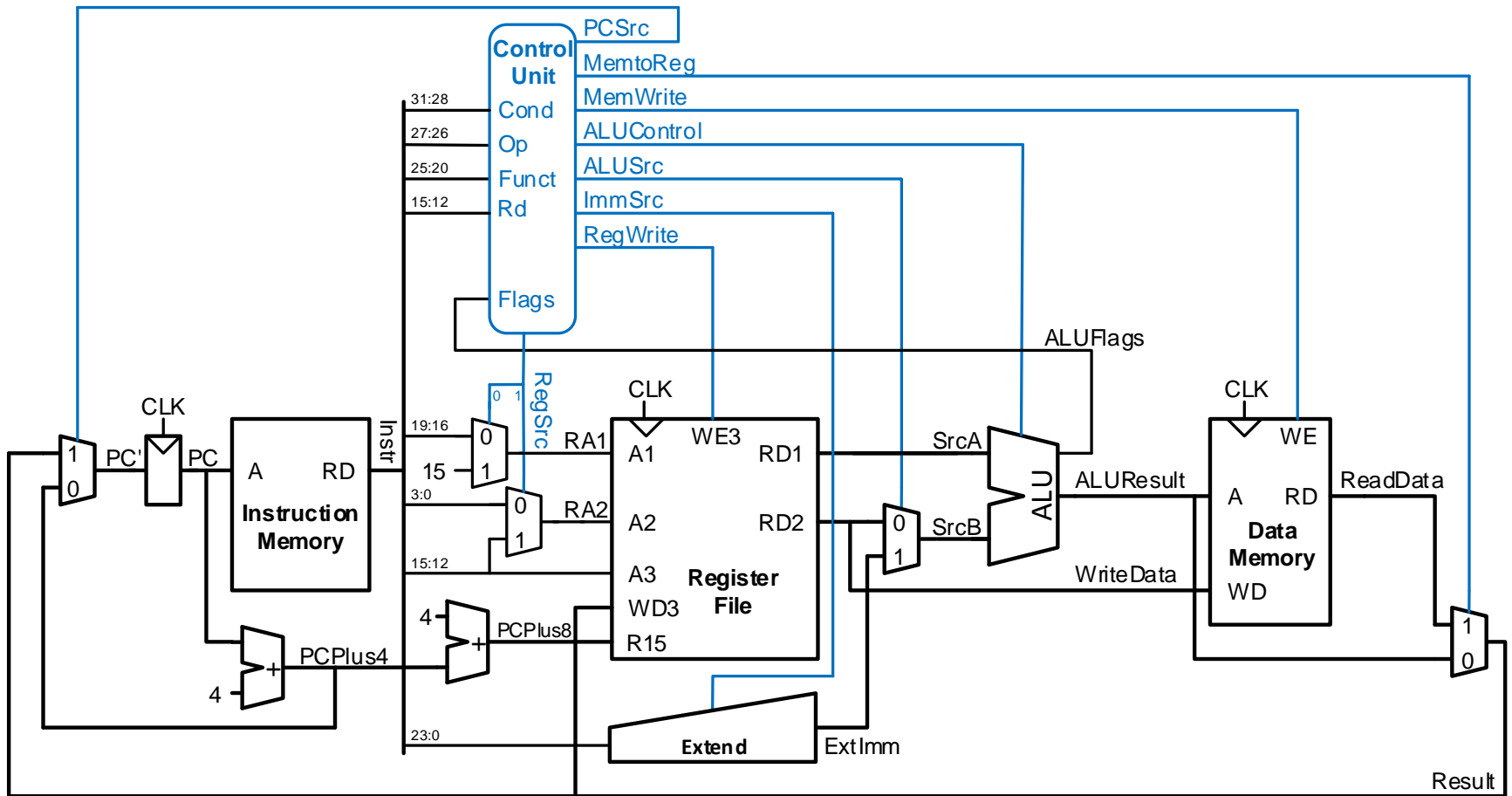


Single-Cycle Control

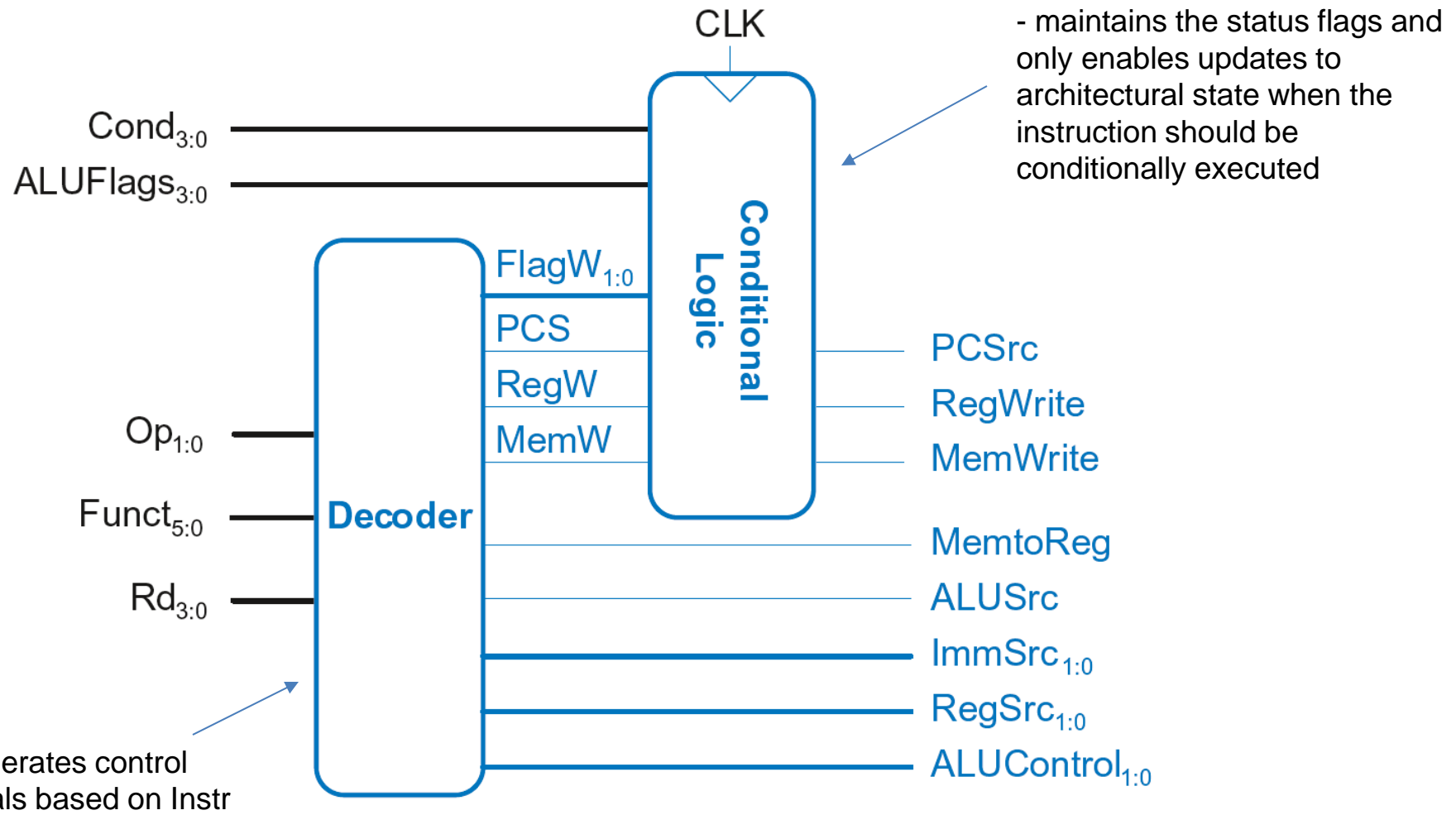


Single-Cycle Control

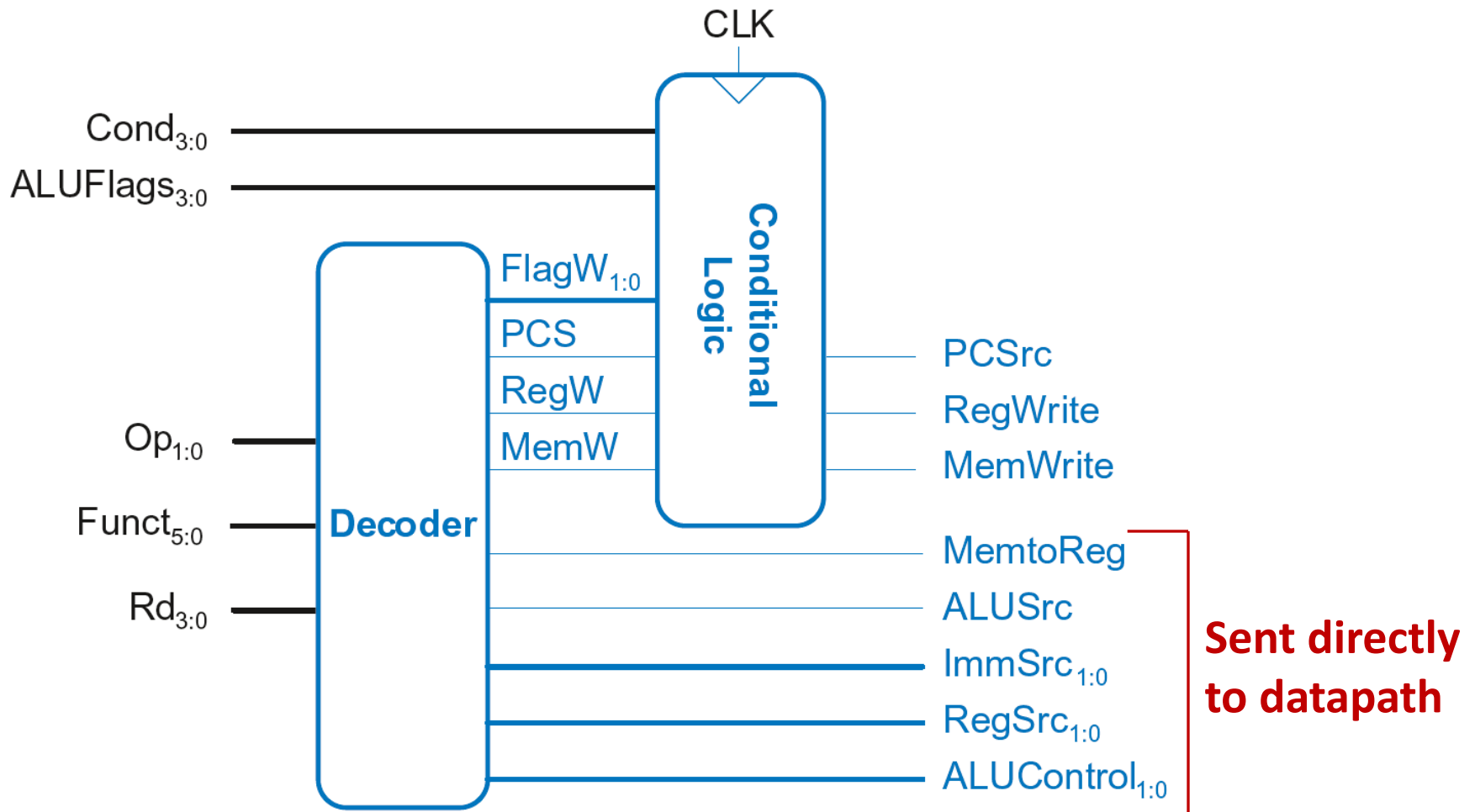

Single-Cycle Control

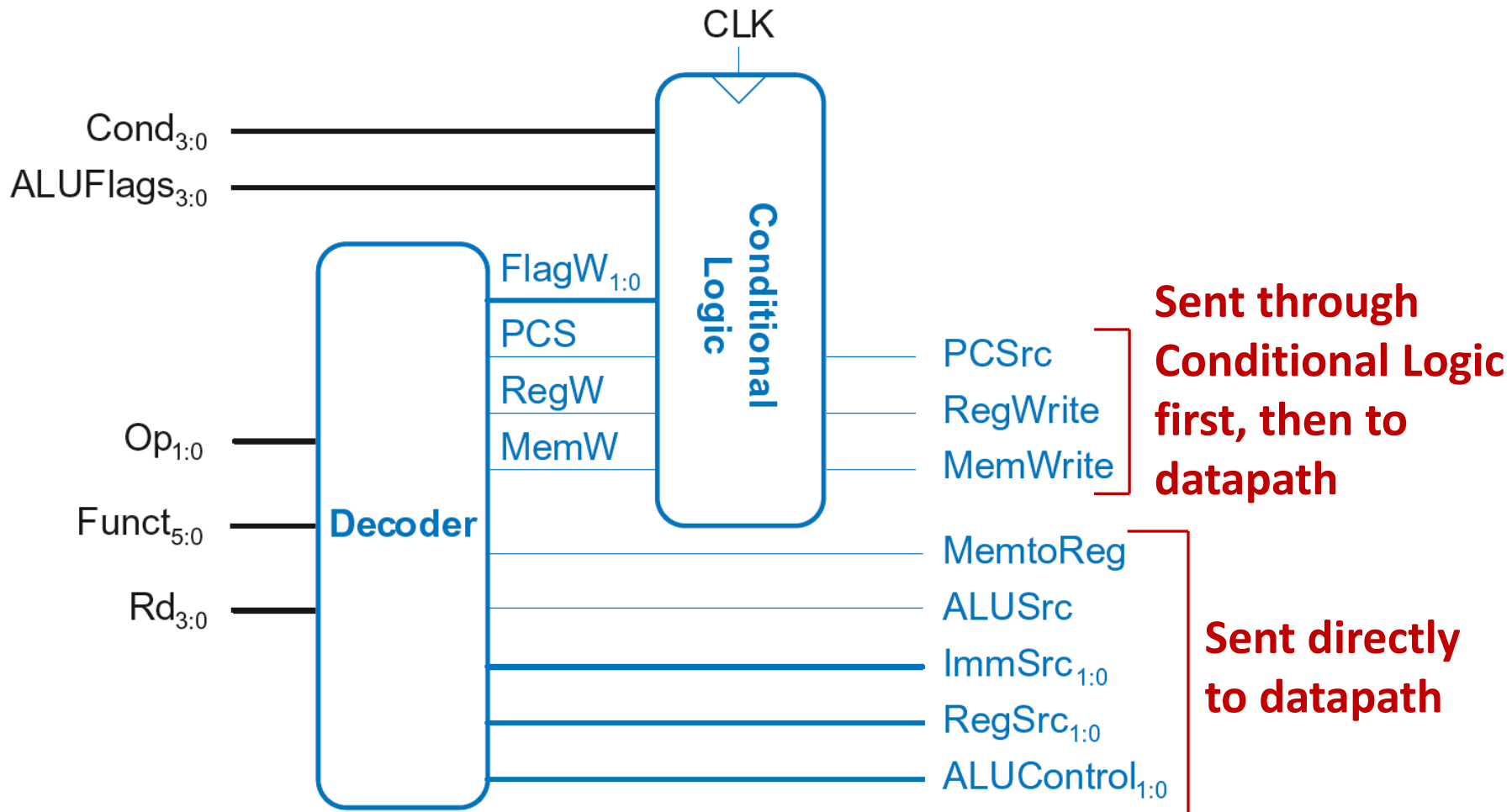


Single-Cycle Control

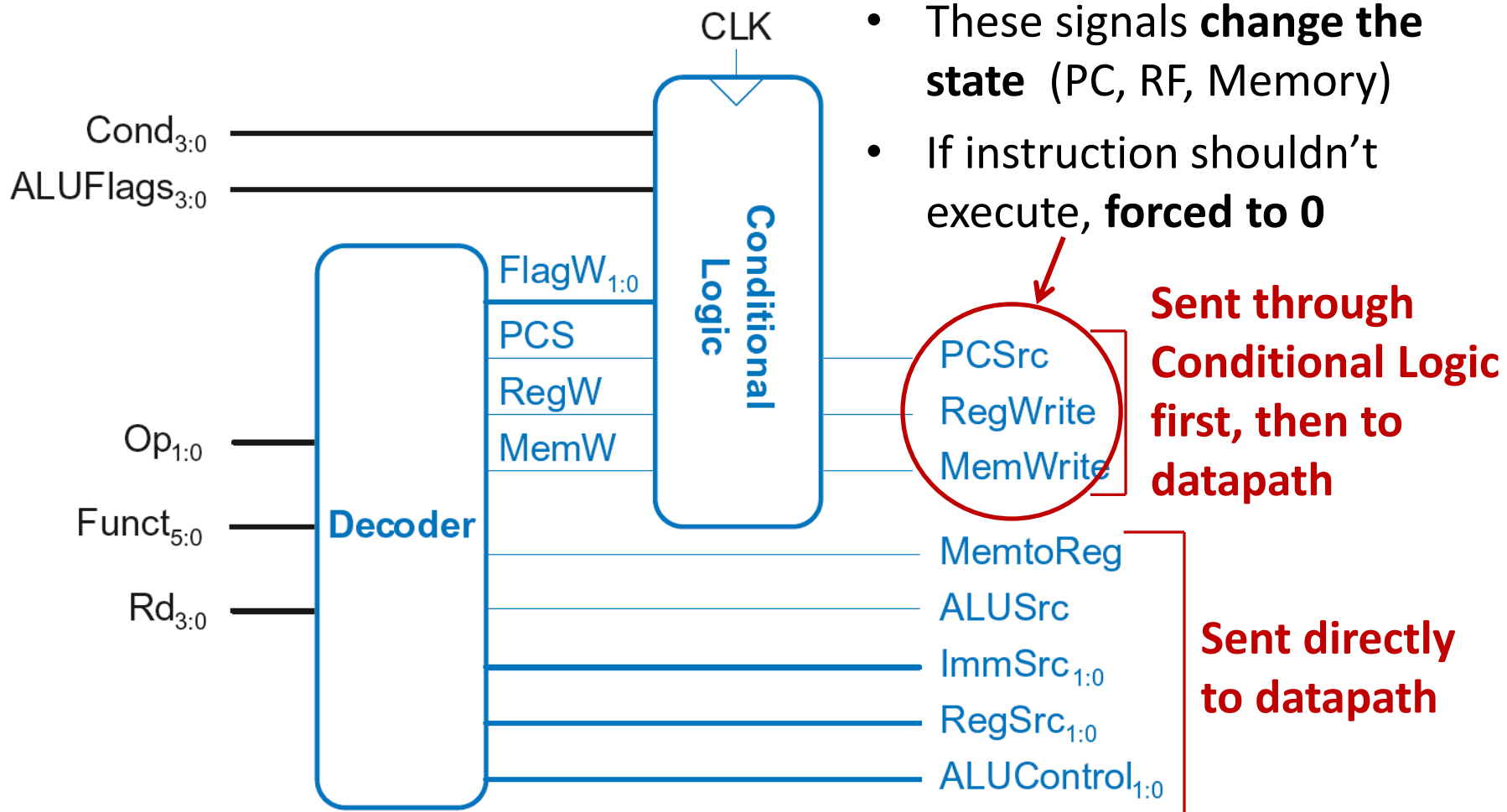


- These signals **change the state** (PC, RF, Memory)
- If instruction shouldn't execute, **forced to 0**

Single-Cycle Control

 


- **$FlagW_{1:0}$** : Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with $S=1$)

Single-Cycle Control

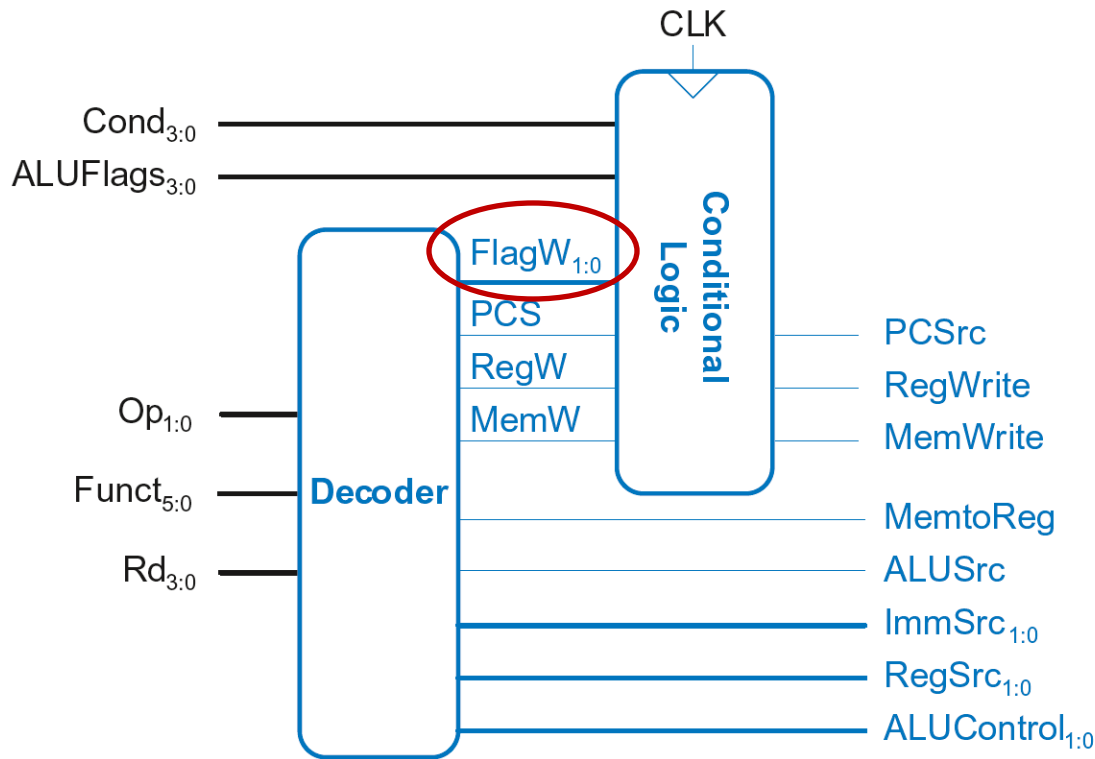


- **$FlagW_{1:0}$** : Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags

Single-Cycle Control

 


- **$FlagW_{1:0}$** : Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags
- So, two bits needed:
 - $FlagW_1 = 1$** : NZ saved (*ALUFlags_{3:2}* saved)
 - $FlagW_0 = 1$** : CV saved (*ALUFlags_{1:0}* saved)

Single-Cycle Control

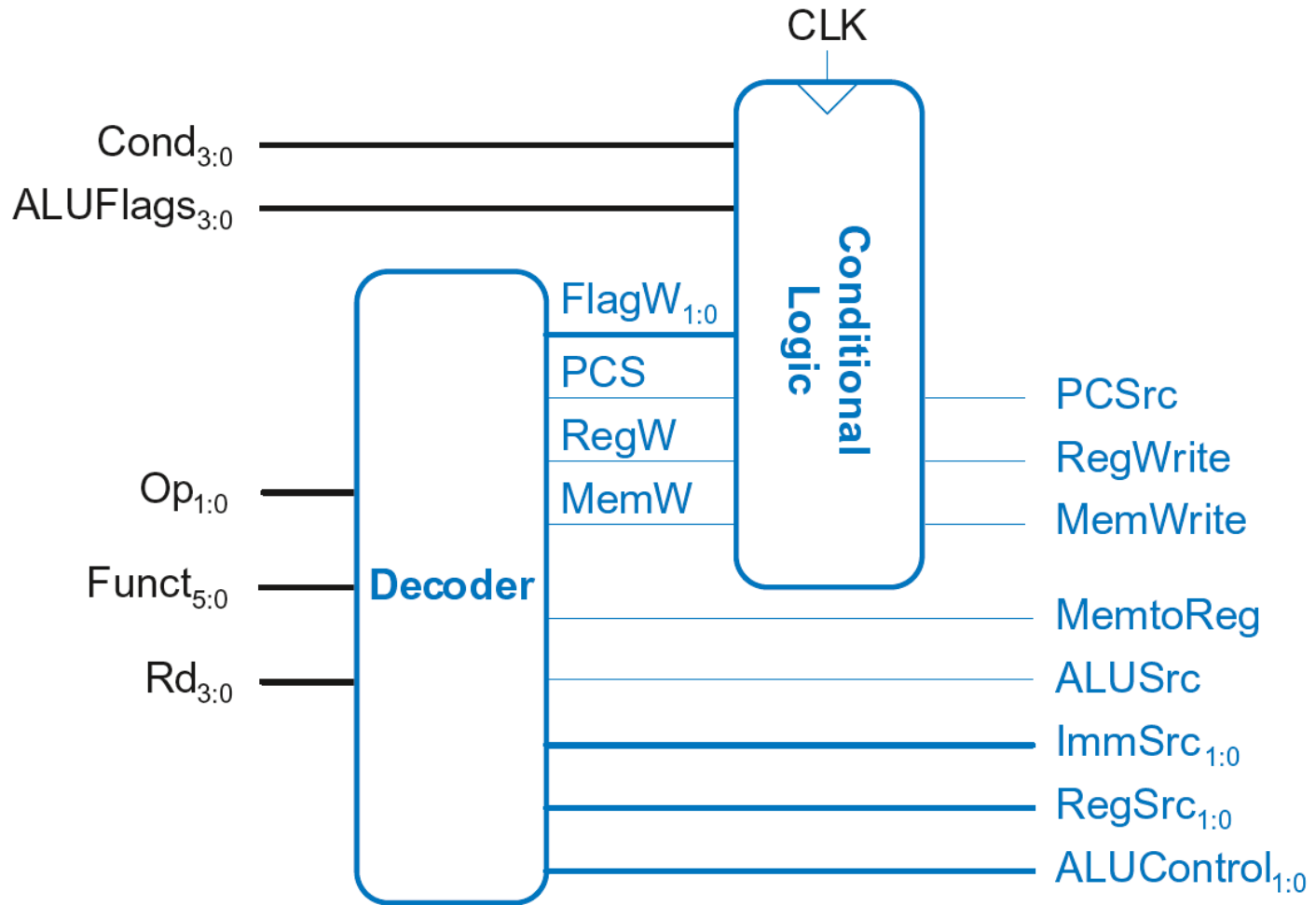


Single-Cycle Control: Decoder

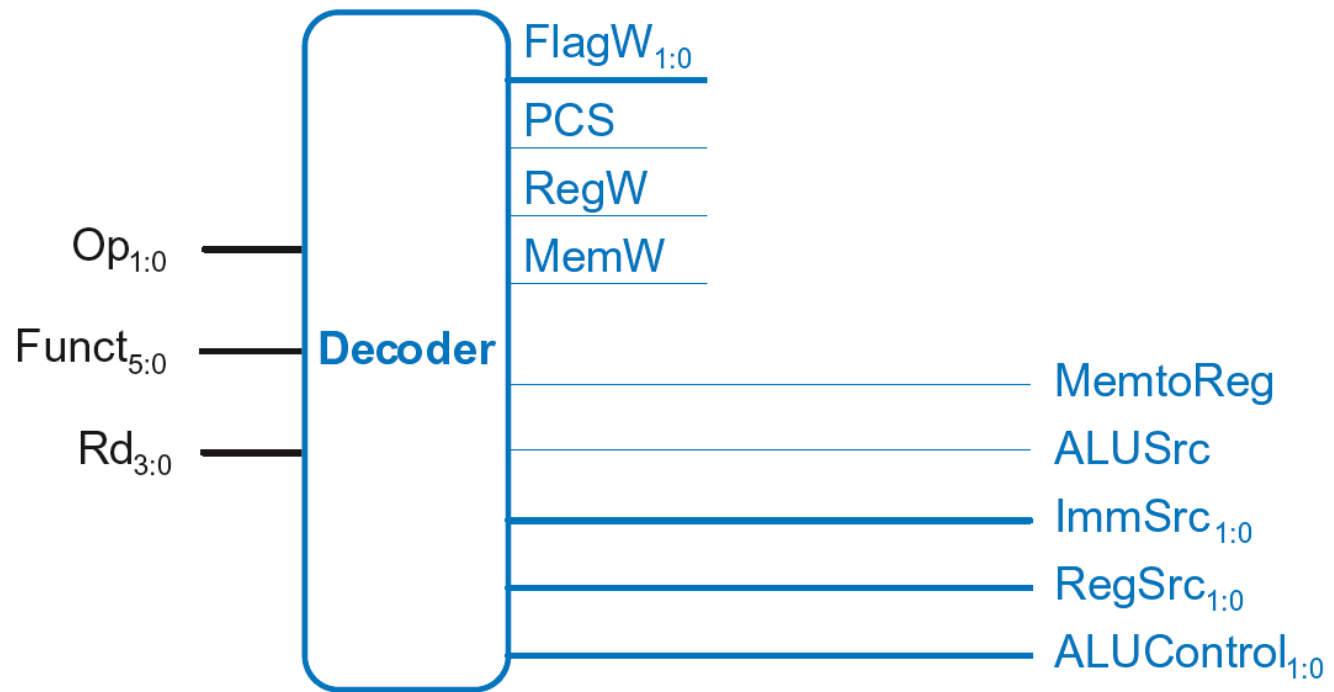

Single-Cycle Control: Decoder

Submodules:


- Main Decoder
- ALU Decoder
- PC Logic

 

Single-Cycle Control: Decoder

Submodules:

 
- **Main Decoder**
- ALU Decoder
- PC Logic



Control Unit: Main Decoder

Op	Funct ₅	Funct ₀	Type	Branch	MentoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
11	X	X	B	1	0	0	1	10	0	X1	0


Single-Cycle ARM Processor

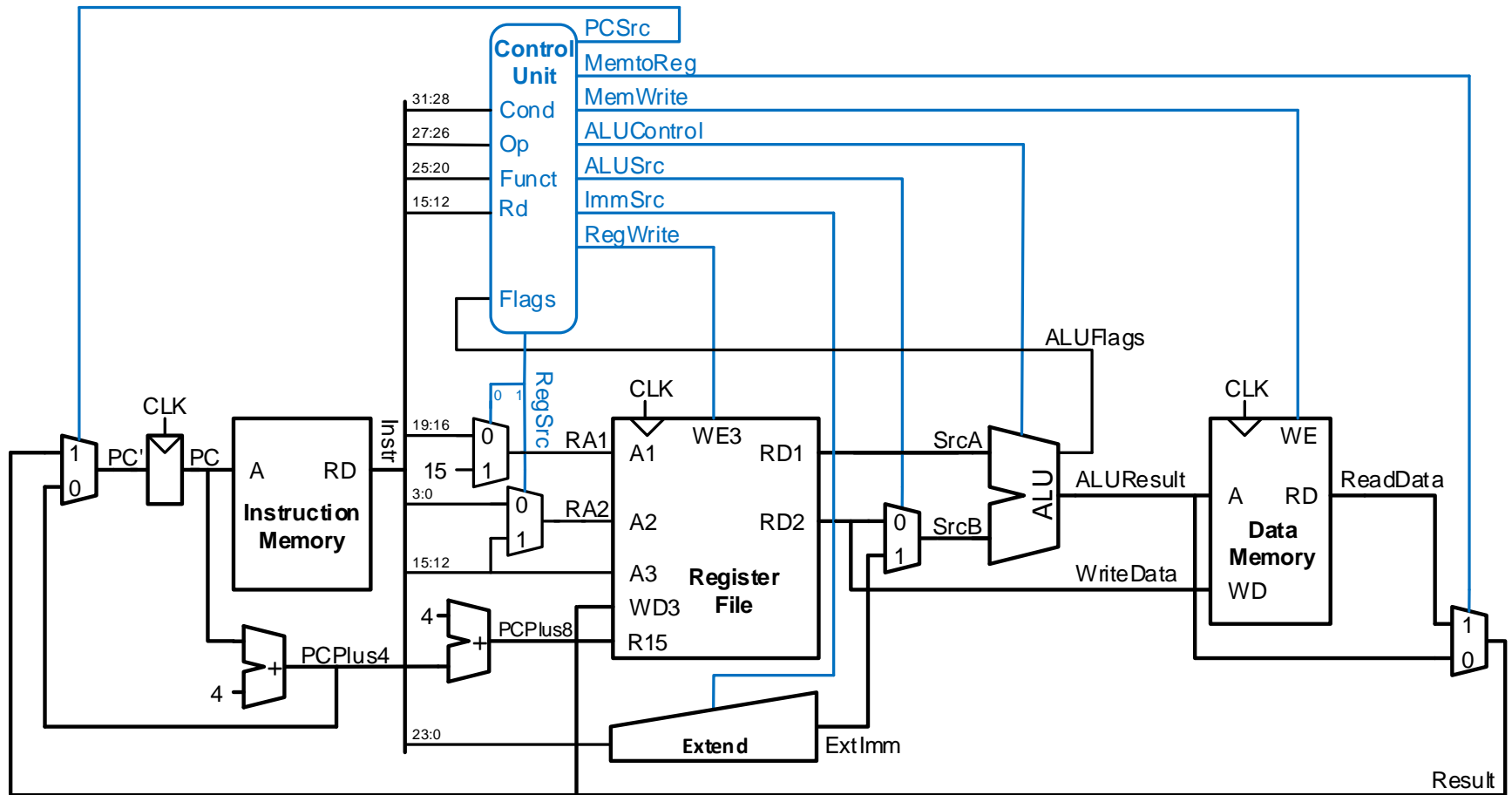

Single-Cycle Control: Decoder


Submodules:

 - Main Decoder
- **ALU Decoder**
- PC Logic




Review: ALU

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

 


Review: ALU

 

Single-Cycle Control: Decoder

Submodules:

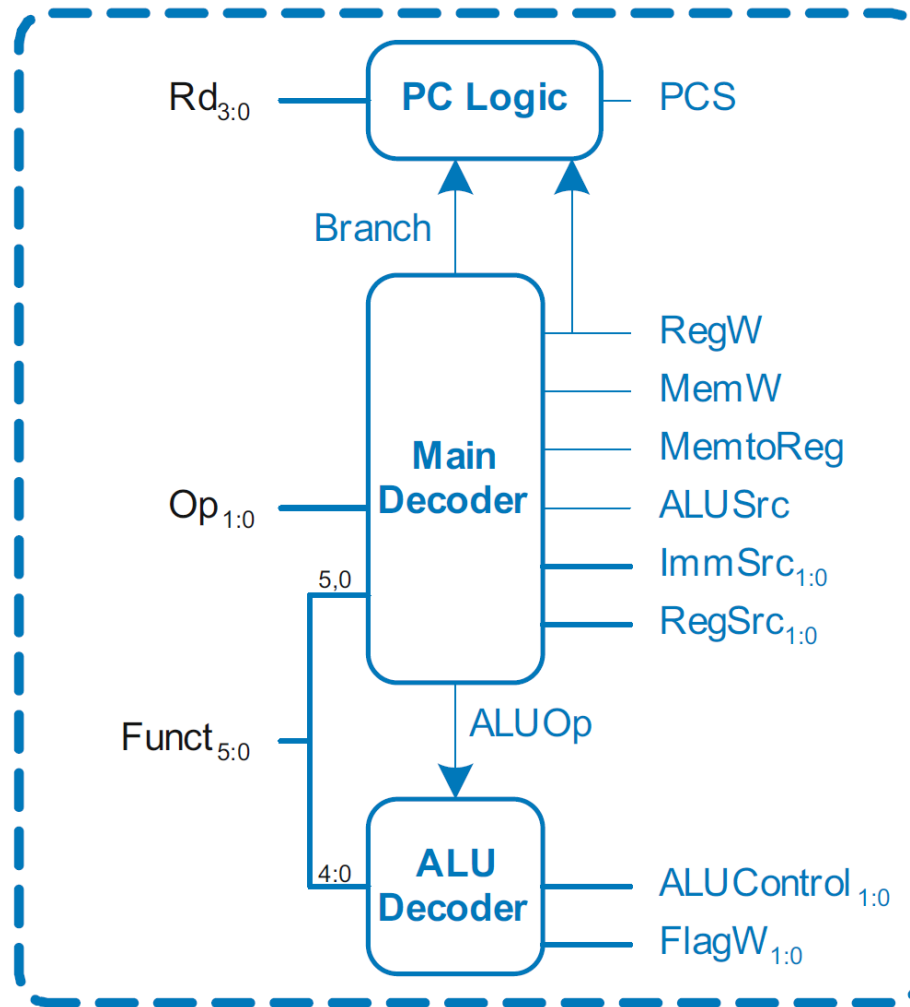- Main Decoder
- **ALU Decoder**
- PC Logic



Control Unit: ALU Decoder


ALUOp	Func _{4:1} (cmd)	Func ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

- **FlagW₁** = 1: NZ (Flags_{3:2}) should be saved
- **FlagW₀** = 1: CV (Flags_{1:0}) should be saved

Single-Cycle Control: Decoder

Submodules:

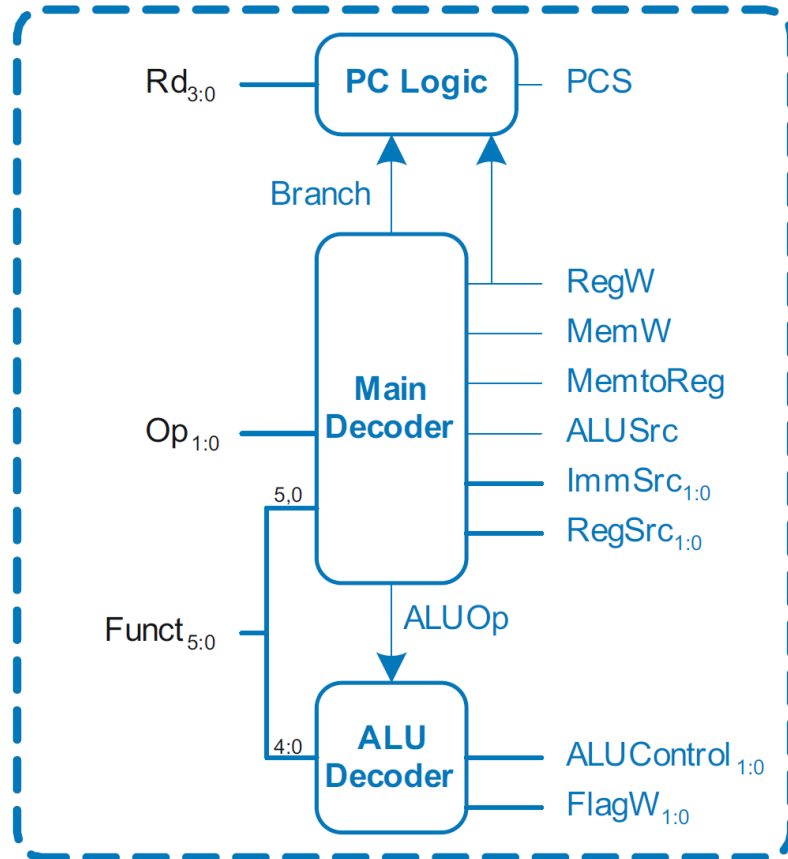- Main Decoder
- ALU Decoder
- **PC Logic**




$$PCS = ((Rd == 15) \& RegW) \mid Branch$$

Single-Cycle Control: PC Logic

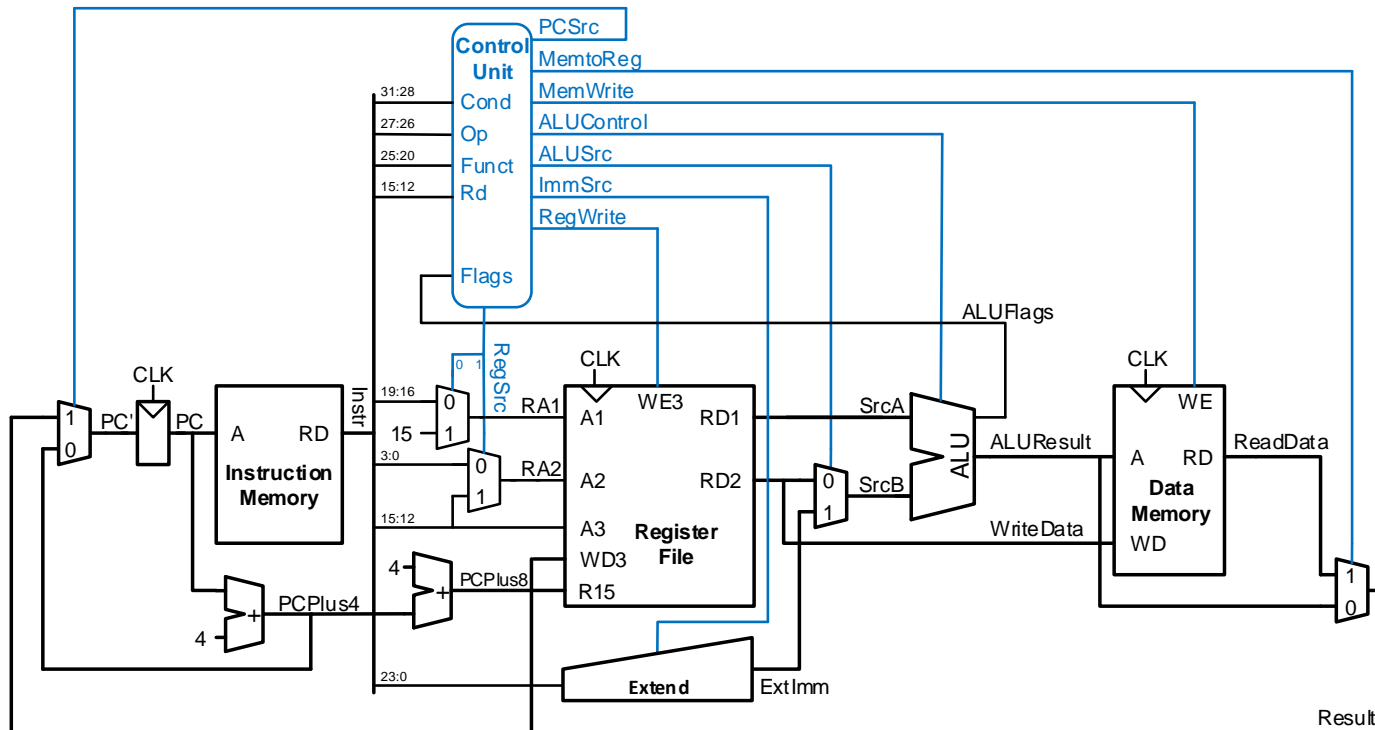
***PCS* = 1 if PC is written by an instruction or branch (B):**

$$PCS = ((Rd == 15) \& RegW) \mid Branch$$




if instruction is to be executed: ***PCSrc* = *PCS***
else ***PCSrc* = 0** (i.e., ***PC* = *PC* + 4**)


Single-Cycle Control

 

Single-Cycle Control: Cond. Logic

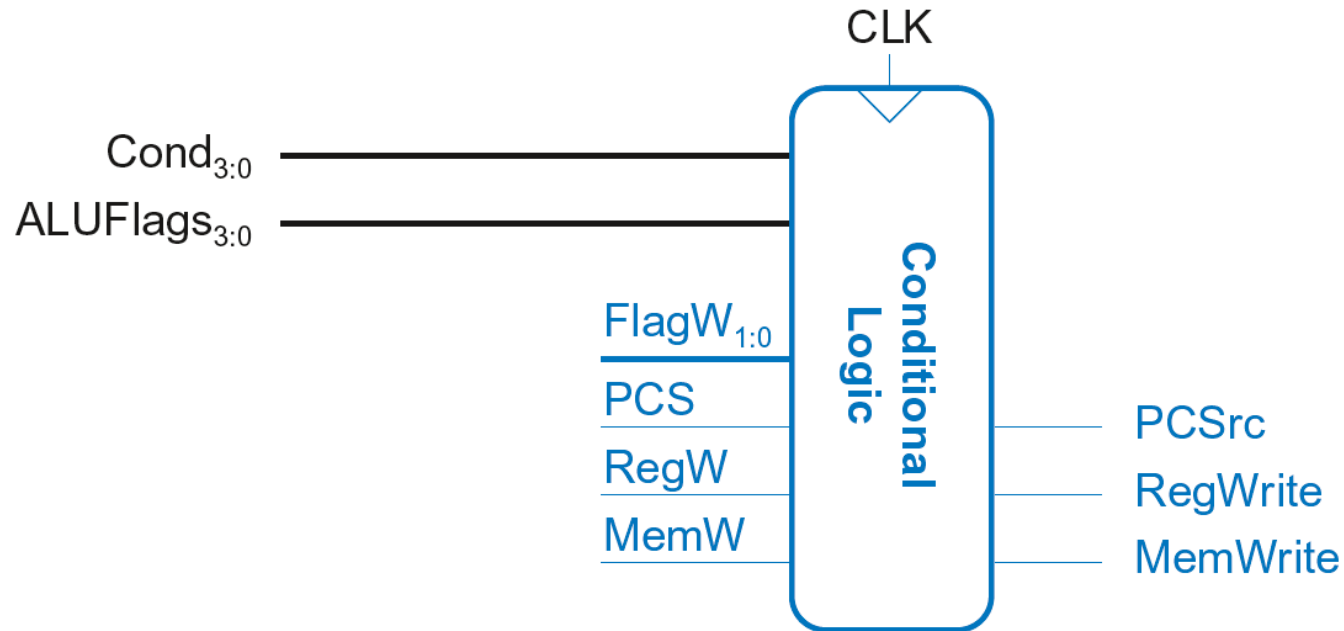


Conditional Logic

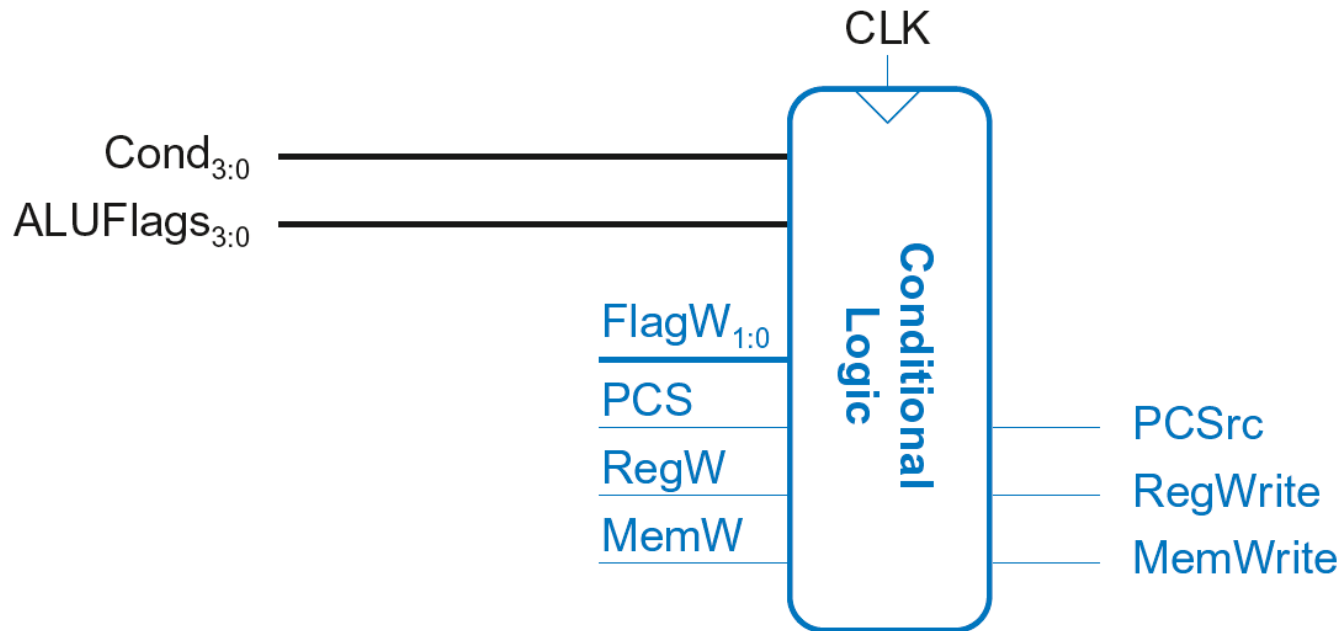

Function:

1. Check if instruction should execute
(if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags3:0)


Conditional Logic

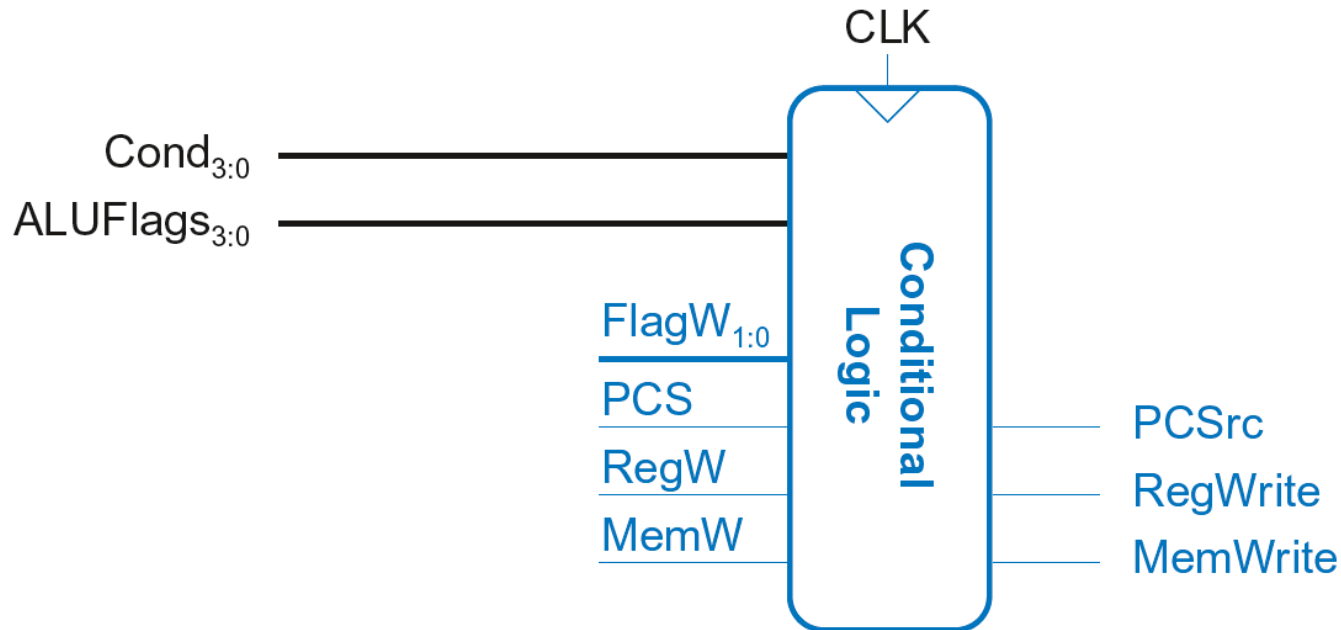


Function:

1. Check if instruction should execute
(if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags3:0)

Single-Cycle Control: Conditional Logic

 


Conditional Logic: Conditional Execution

 

Depending on condition mnemonic (**Cond_{3:0}**) and condition flags (**Flags_{3:0}**) the instruction is executed (**CondEx = 1**)

Conditional Logic: Conditional Execution

Flags_{3:0} is the
status register

 


Depending on condition mnemonic (**Cond_{3:0}**) and condition flags (**Flags_{3:0}**) the instruction is executed (**CondEx = 1**)

Review: Condition Mnemonics

cond	Mnemonic	Name	CondEx
0000	EQ	Equal	Z
0001	NE	Not equal	\bar{Z}
0010	CS/HS	Carry set / unsigned higher or same	C
0011	CC/LO	Carry clear / unsigned lower	\bar{C}
0100	MI	Minus / negative	N
0101	PL	Plus / positive or zero	\bar{N}
0110	VS	Overflow / overflow set	V
0111	VC	No overflow / overflow clear	\bar{V}
1000	HI	Unsigned higher	$\bar{Z}C$
1001	LS	Unsigned lower or same	$Z \text{ OR } \bar{C}$
1010	GE	Signed greater than or equal	$\bar{N} \oplus \bar{V}$
1011	LT	Signed less than	$N \oplus V$
1100	GT	Signed greater than	$\bar{Z}(\bar{N} \oplus \bar{V})$
1101	LE	Signed less than or equal	$Z \text{ OR } (N \oplus V)$
1110	AL (or none)	Always / unconditional	Ignored

Conditional Logic: Conditional Execution

Flags_{3:0} = NZCV

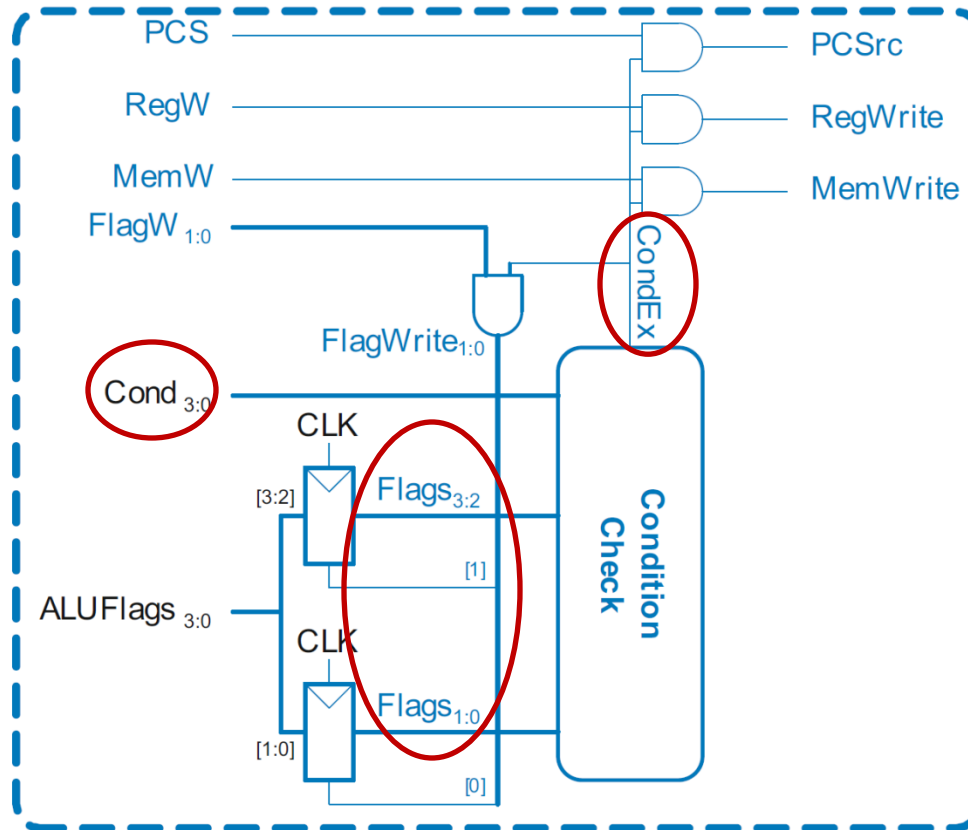

Example:


AND R1, R2, R3

Cond_{3:0} = 1110 (unconditional)

=> **CondEx = 1**

Conditional Logic: Conditional Execution

$\text{Flags}_{3:0} = \text{NZCV}$

 


Example:

`EOREQ R5, R6, R7`

$\text{Cond}_{3:0} = 0000$ (EQ): if $\text{Flags} = \text{x1xx}$ \Rightarrow **CondEx** = 1

Conditional Logic

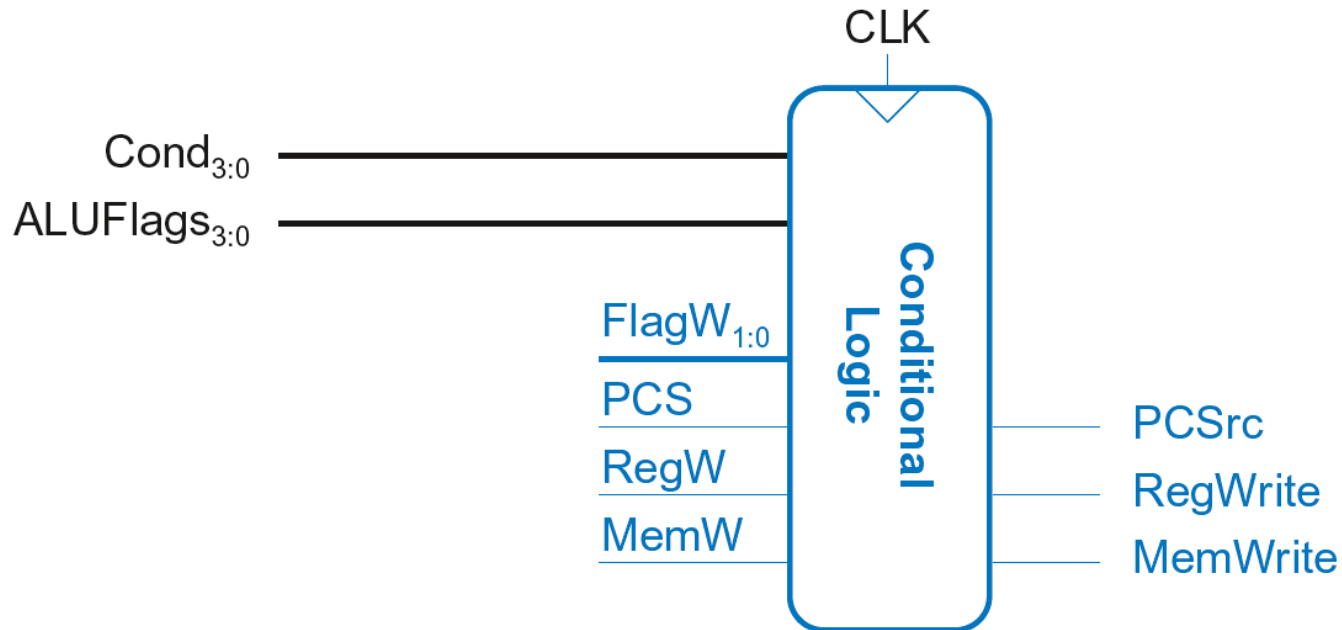


Function:

1. Check if instruction should execute
(if not, force PCSrc, RegWrite, and MemWrite to 0)
2. **Possibly update Status Register (Flags3:0)**

Conditional Logic: Update (Set) Flags


$\text{Flags}_{3:0} = \text{NZCV}$

 

$\text{Flags}_{3:0}$ **updated** (with $\text{ALUFlags}_{3:0}$) if:

- **FlagW** is 1 (i.e., the instruction's S-bit is 1) AND
- **CondEx** is 1 (the instruction should be executed)

Conditional Logic: Update (Set) Flags

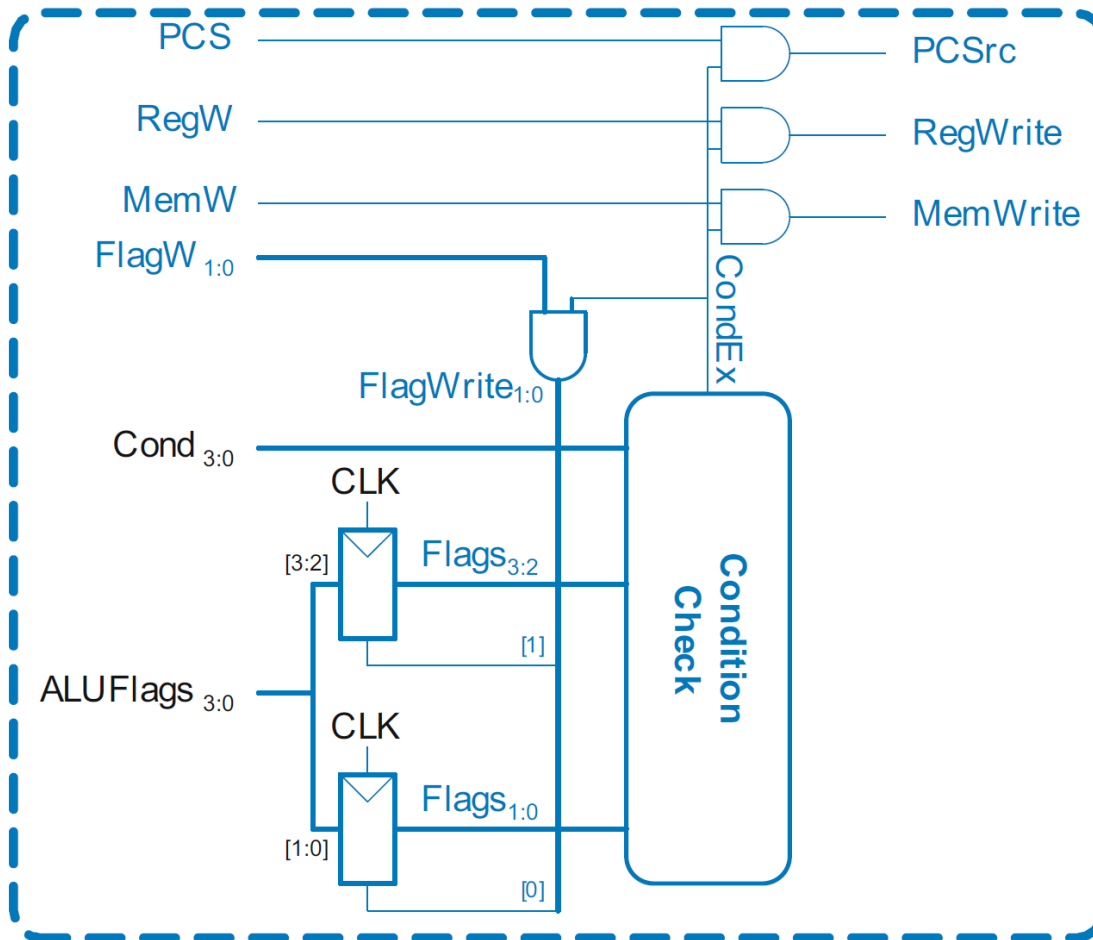

Recall:

- ADD, SUB update **all** Flags
- AND, OR update **NZ only**
- So Flags status register has two write enables:
FlagW_{1:0}


Review: ALU Decoder

ALUOp	Func _{4:1} (cmd)	Func ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

- **FlagW₁** = 1: NZ (Flags_{3:2}) should be saved
- **FlagW₀** = 1: CV (Flags_{1:0}) should be saved

Conditional Logic: Update (Set) Flags

All Flags
updated

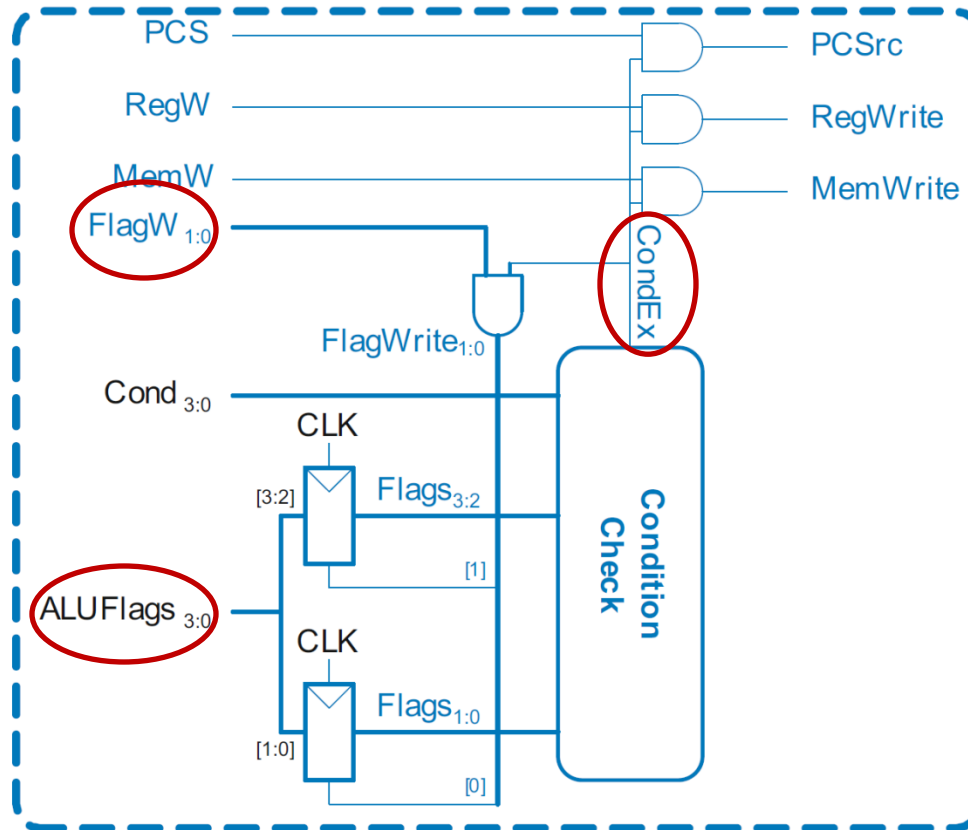


Example: SUBS R5, R6, R7

FlagW_{1:0} = 11 AND CondEx = 1 (unconditional) => FlagWrite_{1:0} = 11

Conditional Logic: Update (Set) Flags

Flags_{3:0} = NZCV

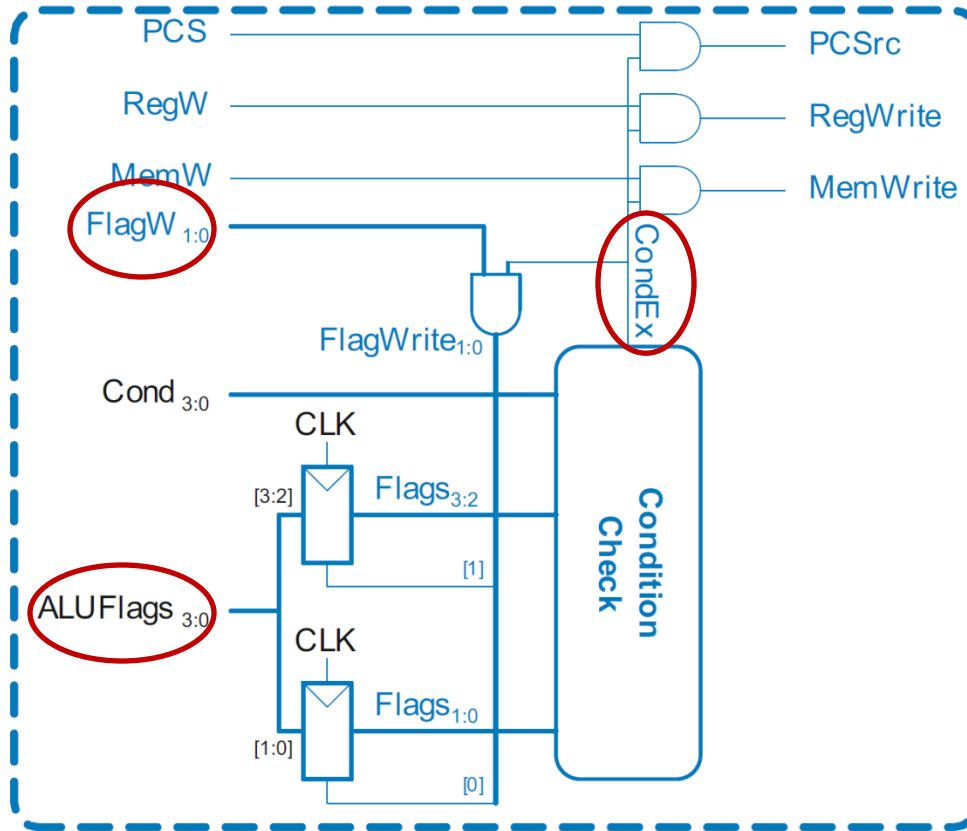- Only **Flags_{3:2}** updated
- i.e., only **NZ** Flags updated




Example: ANDS R7, R1, R3

FlagW_{1:0} = 10 AND **CondEx** = 1 (unconditional) => **FlagWrite**_{1:0} = 10


Example: ORR

Op	Funct ₅	Funct ₀	Type	Branch	MemoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1

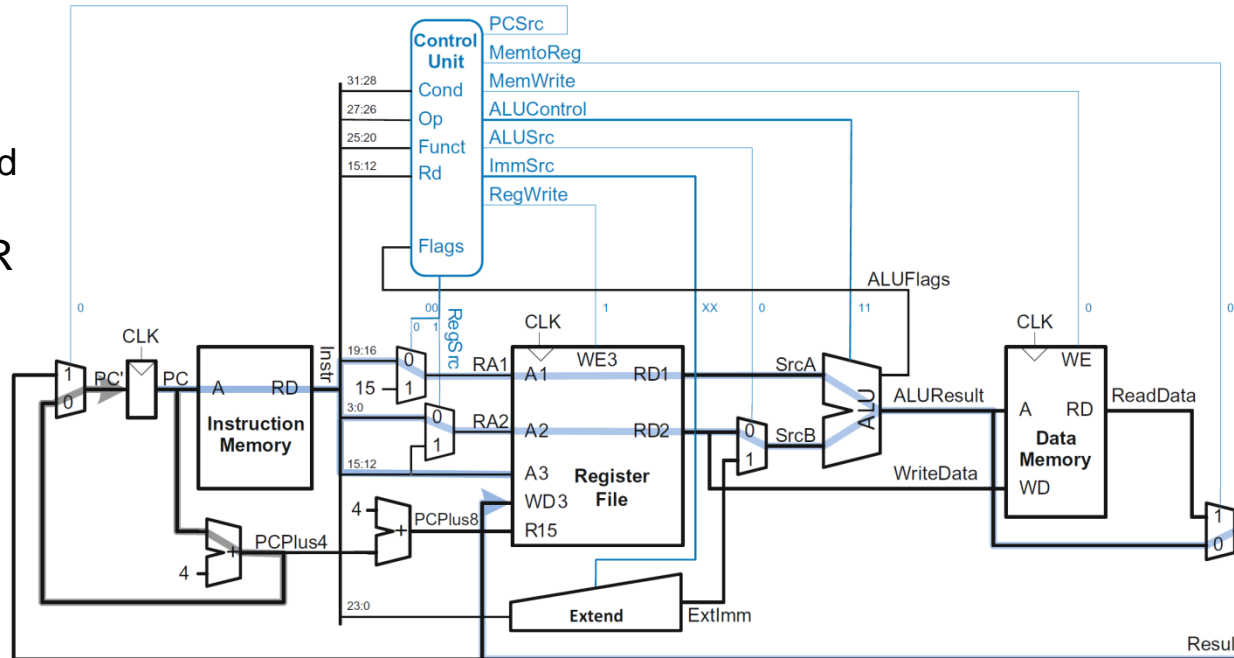Control signals and data flow while executing an ORR instruction




Example: ORR

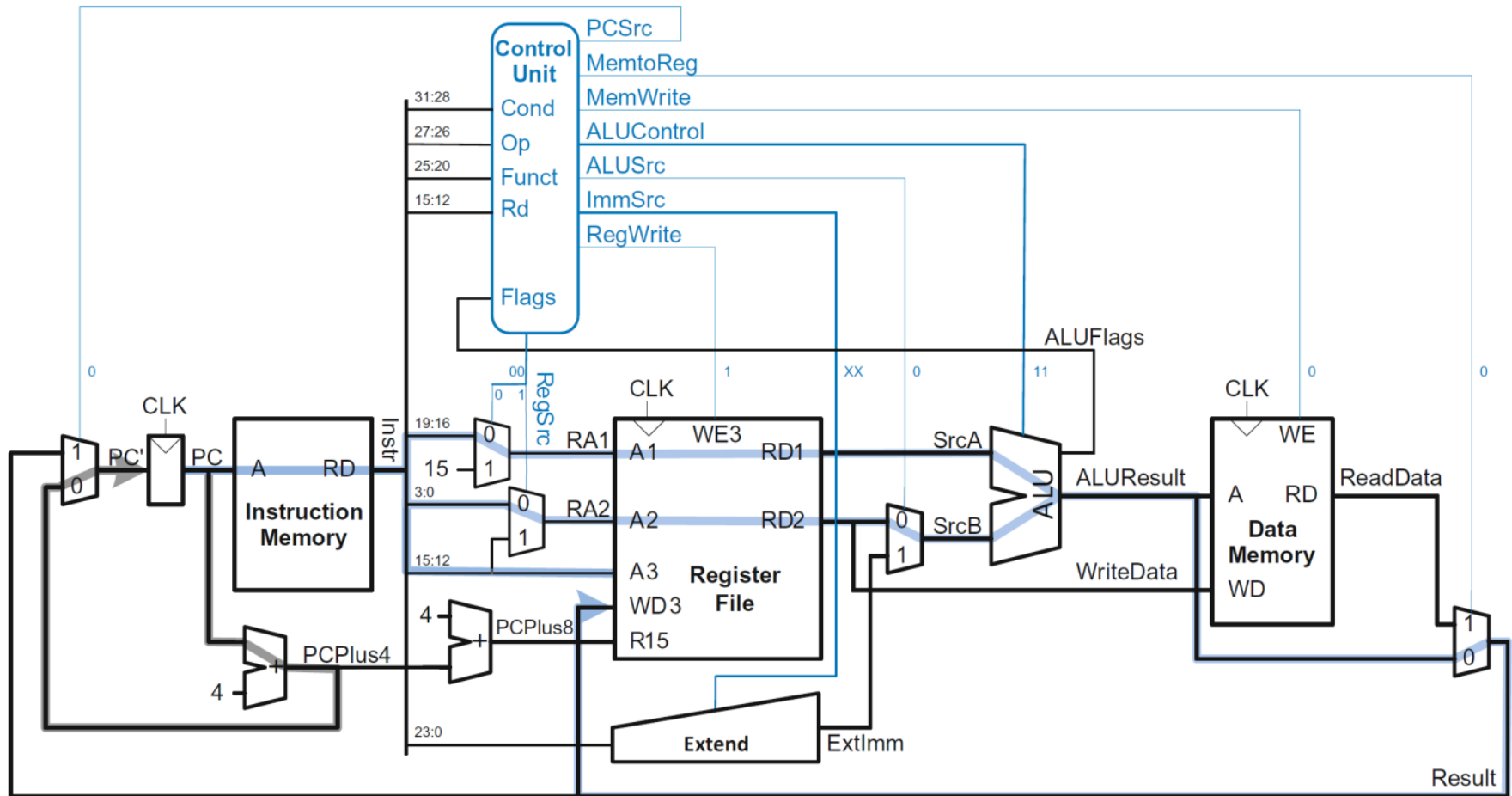


More Instructions

- We have considered a limited subset of the full ARM instruction set.
- In the following slides, we consider
 - adding *compare (CMP)* instruction
 - supporting addressing modes in which the second source is a shifted register.
- With enough effort, one can extend the single-cycle processor to handle every ARM instruction.
- Supporting some instructions simply requires enhancing the decoders, whereas supporting others also requires new hardware in the datapath.

Extended Functionality: CMP

 


Extended Functionality: CMP

 

No change to datapath


Extended Functionality: CMP

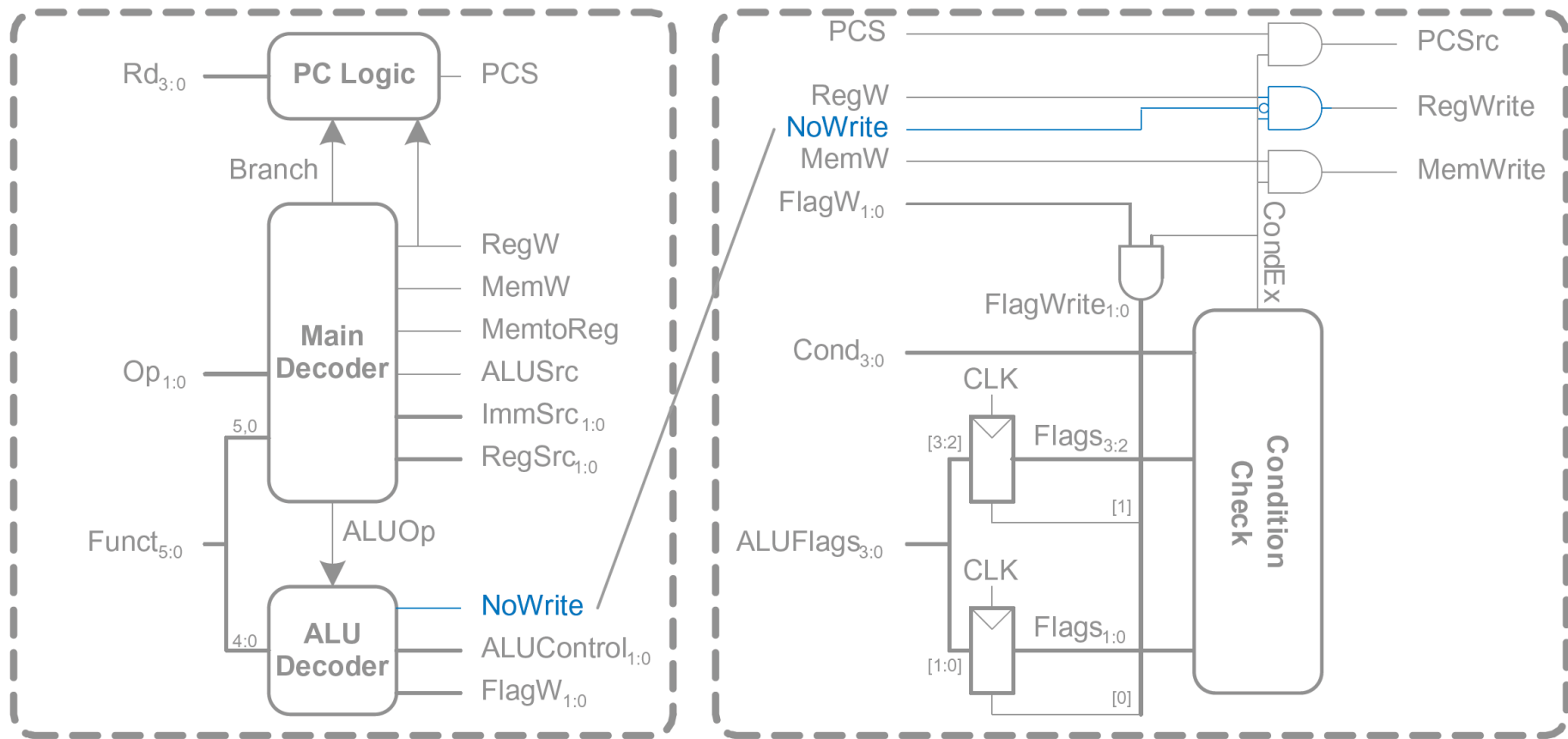

Extended Functionality: CMP

ALUOp	Func _{4:1} (cmd)	Func ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}	NoWrite
0	X	X	Not DP	00	00	0
1	0100	0	ADD	00	00	0
		1			11	0
	0010	0	SUB	01	00	0
		1			11	0
	0000	0	AND	10	00	0
		1			10	0
	1100	0	ORR	11	00	0
		1			10	0
	1010	1	CMP	01	11	1


Extended Functionality: Shifted Register

 

ADD R7, R2, R12, LSR #5

31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0
14	0	0	4	0	2	7	5	01 ₂	0	12
cond	op	I	cmd	S	rn	rd	shamt5	sh		rm

Extended Functionality: Shifted Register

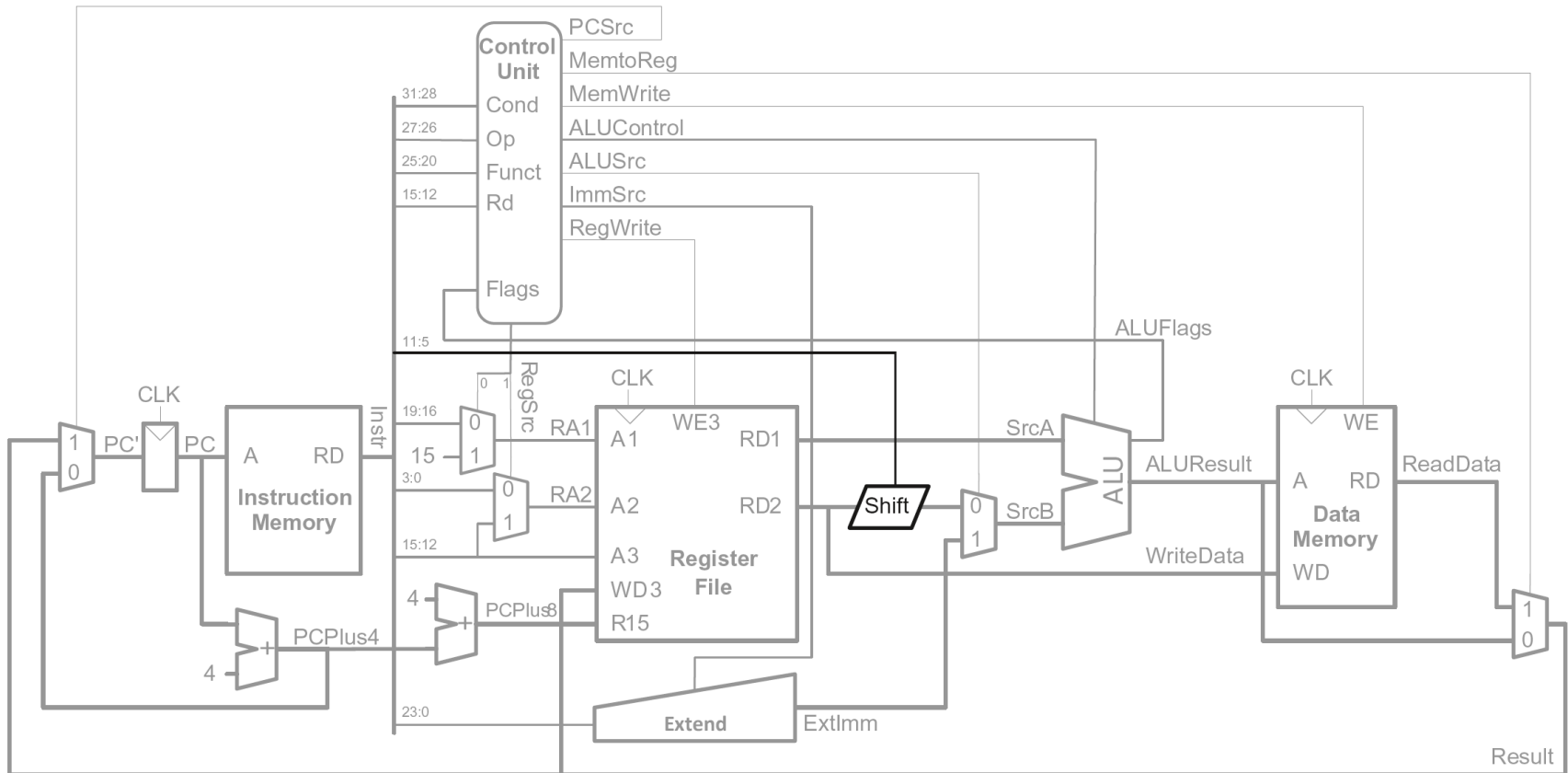

No change to controller


Review: Processor Performance

Program Execution Time

$$= (\text{\#instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \text{\# instructions} \times \text{CPI} \times T_c$$

Single-Cycle Performance

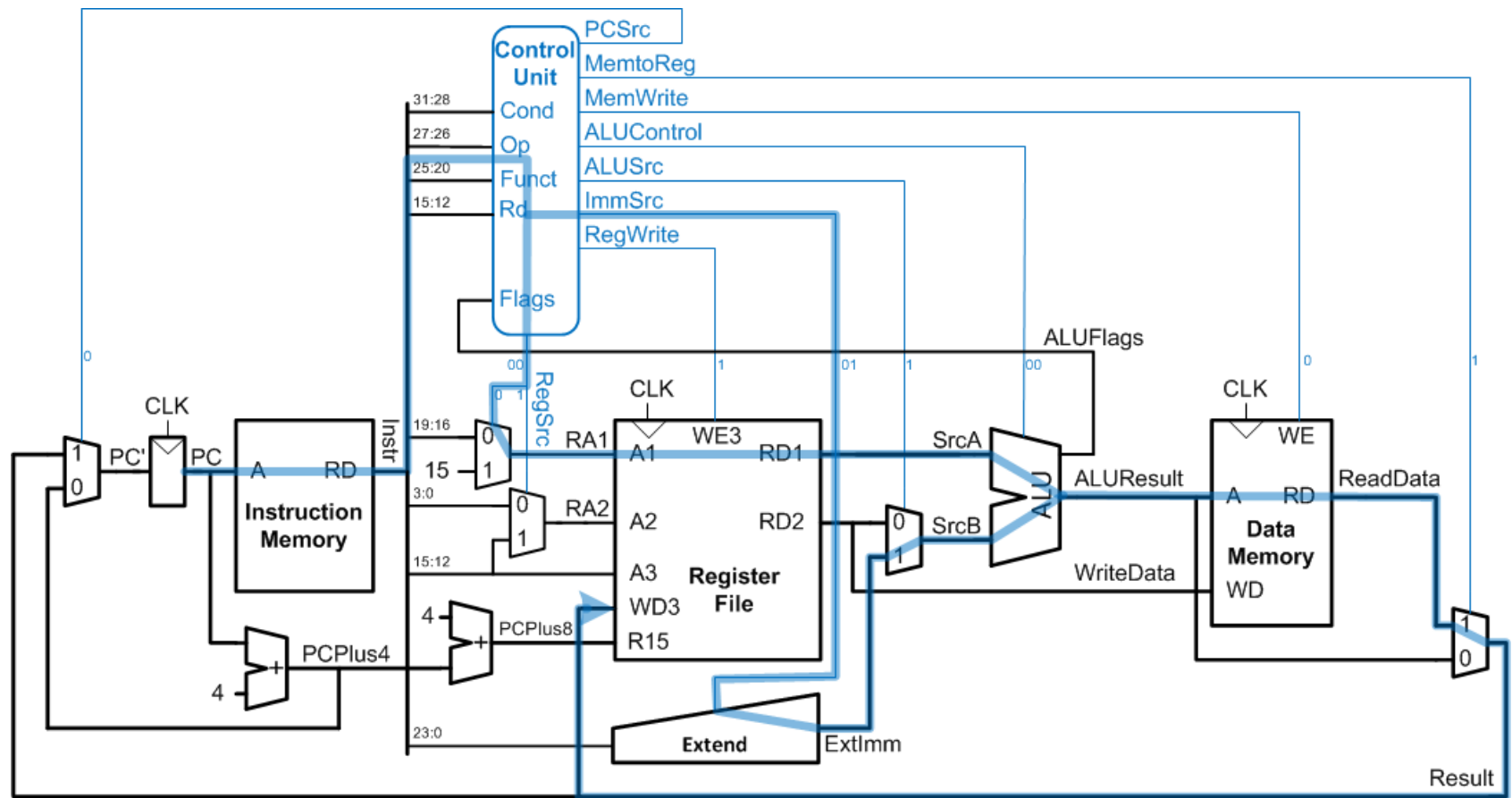

T_c limited by critical path (LDR)

Single-Cycle Performance

- **Single-cycle critical path:**

$$T_{cl} = t_{pcq_PC} + t_{mem} + t_{dec} + \\ \max[t_{mux} + t_{RFread}, t_{sext} + t_{mux}] + \\ t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- **Typically, limiting paths are:**

- memory, ALU, register file

- $T_{cl} = t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$

assuming $t_{RFread} > t_{sext}$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{cl} = ?$$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned}T_{cl} &= t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\&= [50 + 2(200) + 70 + 100 + 120 + 2(25) + 60] \text{ ps} \\&= \mathbf{840 \text{ ps}}\end{aligned}$$

Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1)(840 \times 10^{-12} \text{ s}) \\ &= \mathbf{84 \text{ seconds}}\end{aligned}$$